

# Overflow

- ▶ When we use fixed size Register for arithmetic operands there is the hazard at each micro-ops of overflow.
- ▶ If Register R stores an n-bit 2's complement number, then:

$$-2^{n-1} \leq R \leq 2^{n-1}-1$$


- ▶ Note the asymmetry, so even negation can cause overflow, e.g.

$$R \leftarrow -2^{n-1} \text{ then } R \leftarrow -R \Rightarrow \text{OVERFLOW}$$
 
# Carry and Overflow

- We can detect overflow for all the previous operations simply by recording the status bits  $C$  = Carry and  $V$  = Overflow (see section 3.10 I Mano and Kime).

$$K_1: C \leftarrow C_n, V \leftarrow C_n \oplus C_{n-1}$$



# Adder-Subtractor


- ▶ This then is the basis for the adder-subtractor on the next page which uses control input  $X$  to select addition and  $X$  for subtraction.

$$\bar{X}.K_1: R1 \leftarrow R1 + R2$$

$$X.K_1: R1 \leftarrow R1 + \overline{R2} + 1$$

$$K_1: C \leftarrow C_n, V \leftarrow C_n \oplus C_{n-1}$$

# Add & Subtract Micro operation

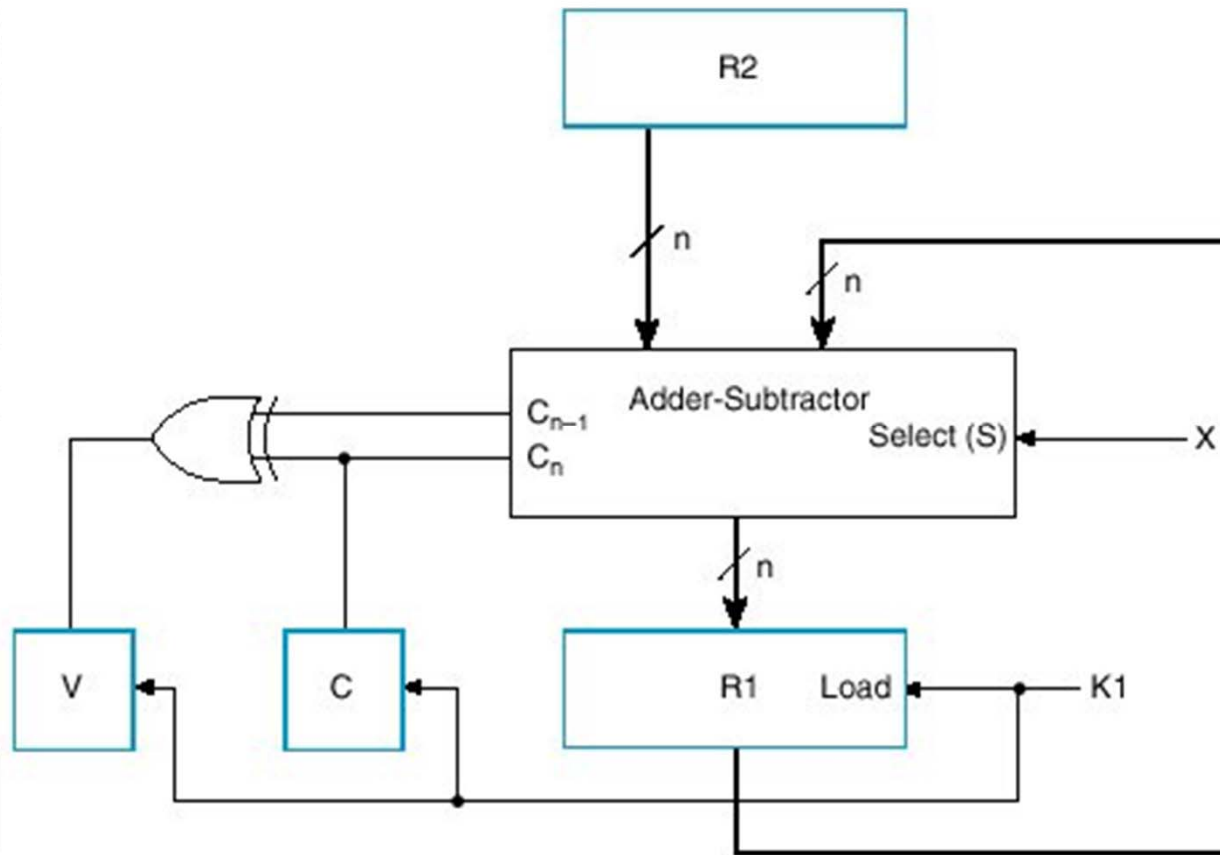



# Logic Micro-operations

▶ The aim here is to provide an effective set of bit-wise functions. A typical basic set follows:

**Symbolic  
micro-op**

**Description**

$R0 \leftarrow \overline{R1}$

Logical bitwise NOT (1's compliment)

$R0 \leftarrow R1 \wedge R2$

Logical bitwise AND (clears bits)

$R0 \leftarrow R1 \vee R2$

Logical bitwise OR (sets bits)

$R0 \leftarrow R1 \oplus R2$

Logical bitwise XOR (complements bits)

^ And v

- ▶ George Bode Prof. Of mathematics in UCC introduced the notation ' $\wedge$ ' and ' $\vee$ ' in 1854, and they are used in Register Transfer (RT) notation if it is necessary to distinguish addition from logical OR. For example:

$K_1 + K_2 : R1 \leftarrow R2 + R3, R4 \leftarrow R5 \vee R6$

Logical OR

Logical OR

addition

- ▶ The OR micro-ops will always use  $\vee$ .

# Shift Micro-operations

- ▶ These provide lateral bitwise shift which are essential for many basic arithmetic algorithms e.g. multiplication division, square root...
- ▶ The minimal set is:

$$\begin{aligned} R \leftarrow sr \ R &\equiv R_i \leftarrow R_{i+1} \ i=0, n-2, R_{n-1} \leftarrow 0 \\ R \leftarrow sl \ R &\equiv R_i \leftarrow R_{i-1} \ i=1, n-1, R_0 \leftarrow 0 \end{aligned}$$

# Logical Shifts

- ▶ These are logical shifts and from them you can develop variants which handle the end bits differently, e.g. arithmetic shift, rotates...
- ▶ Please see table 9-5 in Mano and Kime.



# Transfer Micro-operations

- ▶ Providing choice of path
- ▶ Two approaches are used:
  - ▶ Multiplexer-based transfer for speed
  - ▶ Bus-based transfers for flexibility and economy

# Transfer with Multiplexer

- ▶ The if-then else control structure, when applied to identity micro-ops, results in the destination register requiring selective access to two different source registers.

If ( $K_1=1$ ) then  $R0 \leftarrow R1$   
else if ( $K_2=1$ ) then  $R0 \leftarrow R2$

$K_1: R0 \leftarrow R1, \bar{K}_1 K_2: R0 \leftarrow R2$

# Two Sources - One Destination


► To route two sources to one destination we can use a 2:1 MUX with control input  $S$ , data input  $D0 \wedge D1$ , and  $R0$  must have a load control  $LOAD_{R0}$ .

► From the RT description we deduce the following functions for these control inputs.

$$LOAD_{R0} = K_1 + \bar{K}_1 K_2 = K_1 + K_2$$
$$S = K_1 \Rightarrow D1 = R1 \wedge D0 = R2$$
 
# Multiplexer

From this we derive the circuit schematic, assuming 4-bit Registers.





# Multiplexer Detail

► Note changes in K1 only affect the MUX – R0 path, so transients are short, allowing fast operation.

