

# Shift-and-Add Multiplication ASM

- ▶ Note the concatenation notation
- ▶ From the ASM we can write out the RT description of the system in terms of:
  - ▶ System state
  - ▶ Input signals
- ▶ The table on the following slide allows us to deduce the design of each register:

# Control and Sequencing

- ▶ Two distinct aspects in control unit design
  - ▶ Control of micro-operations
  - ▶ Sequencing
- ▶ We separate the two aspects by providing:
  - ▶ A state table
    - ▶ Defines signals in terms of states and inputs
  - ▶ A simplified ASM chart
    - ▶ Represents only state transitions


# Register Transfers

- ▶ From the ASM we can write out the RT description of the system in terms of:
  - ▶ System state
  - ▶ Input signals
- ▶ By gathering together the RTs loading each register we may easily deduce the design of each register.

# Control Signals for Binary Multiplier

Block Diagram Module	Microoperation	Control Signal Name	Control Expression
Register A:	$A \leftarrow 0$ $A \leftarrow A + B$ $C  A  Q \leftarrow \text{sr } C  A  Q$	Initialize Load Shift_dec	$\text{IDLE} \cdot G$ $\text{MUL0} \cdot Q_0$ $\text{MUL1}$
Register B:	$B \leftarrow IN$	Load_B	LOADB
Flip-Flop C:	$C \leftarrow 0$ $C \leftarrow C_{\text{out}}$	Clear_C Load	$\text{IDLE} \cdot G + \text{MUL1}$ —
Register Q:	$Q \leftarrow IN$ $C  A  Q \leftarrow \text{sr } C  A  Q$	Load_Q Shift_dec	LOADQ —
Counter P:	$P \leftarrow n - 1$ $P \leftarrow P - 1$	Initialize Shift_dec	— —

# Sequencing Part of ASM Chart

 



# Sequence Register and Decoder

► This method uses:

► Sequence Register:

► That holds control states

► Register with  $n$  flop-flops has  $2^n$  states

► Decoder

► Provides output signal for each state.

► An  $n$ -to- $2^n$  decoder has  $2^n$  outputs

# State Table

► Derived from the Sequencing Part of ASM Chart

►  $D_{M0} = \text{IDLE} \cdot G + \text{MUL1} \cdot \bar{Z}$

►  $D_{M1} = \text{MUL0}$

Present state		Inputs		Next state		Decoder Outputs			
Name	$M_1$	$M_0$	G	Z	$M_1$	$M_0$	IDLE	MUL0	MUL1
IDLE	0	0	0	×	0	0	1	0	0
	0	0	1	×	0	1	1	0	0
MUL0	0	1	×	×	1	0	0	1	0
MUL1	1	0	×	0	0	1	0	0	1
	1	0	×	1	0	0	0	0	1
—	1	1	×	×	×	×	×	×	×

# Control Unit for Binary Multiplier

