

# Multiple-Cycle Design


- ▶ The Multiple-Cycle Implementation demonstrates the use of a single memory for:
  - ▶ Data
  - ▶ Instruction
- ▶ This design is also used to show the implementation of more complex instructions

# Memory **M** Address

4	4	3	3	3	3	3	3	3	3	3	3	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0								
Next Address												MS		M	I	P	P	T	T	T	M	FS						M	R	M	M	R	R	R	R	F			
														C	L	I	L	D	A	B	B							D	W	M	W	V	C	N	Z	L			

- ▶ The following address sources are used to fetch:
  - ▶ Instructions -> **PC** Program Counter Register (32bit)
  - ▶ Data -> **Bus A** (32bit)
- ▶ MUX M selects between the two address sources through the **MM** control signal

# PC - Bus A - MM

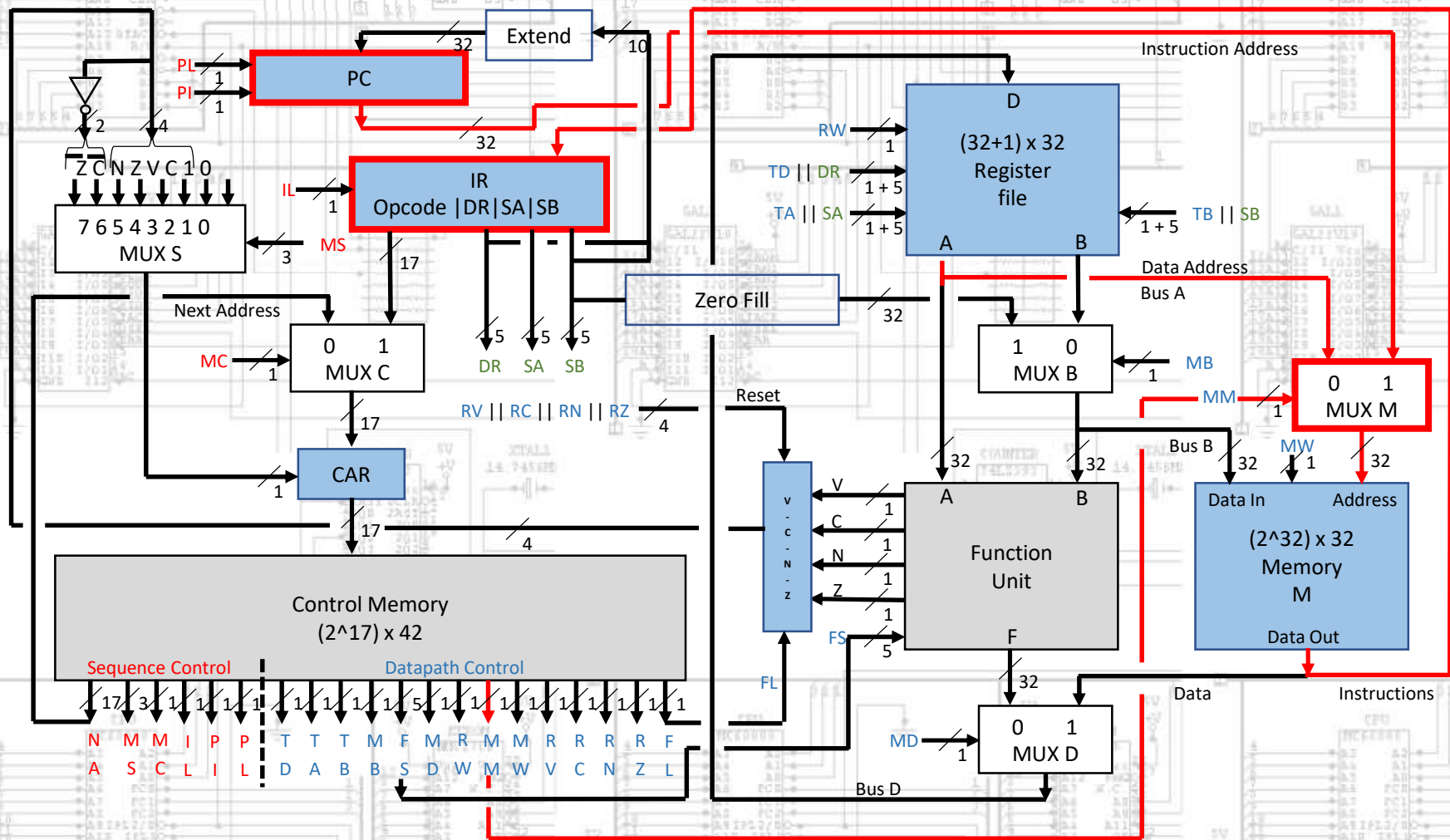


# Temp Register

4	4	3	3	3	3	3	3	3	3	3	3	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0		
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0										
Next Address												MS		M	I	P	P	T	T	T	M	FS					M	R	M	M	R	R	R	R	F						
														C	L	I	L	D	A	B	B						D	W	M	W	V	C	N	Z	L						

- ▶ Instructions are executed over multiple clock cycles
- ▶ This requires an additional register
  - ▶ R32 for temporary storage
- ▶ This register should be selected through an additional bit control signals:
  - ▶ TD, TA, TB
- ▶ The overwrite:
  - ▶ SA, SB, DR



# TD||DR-TA||SA-TB||SB

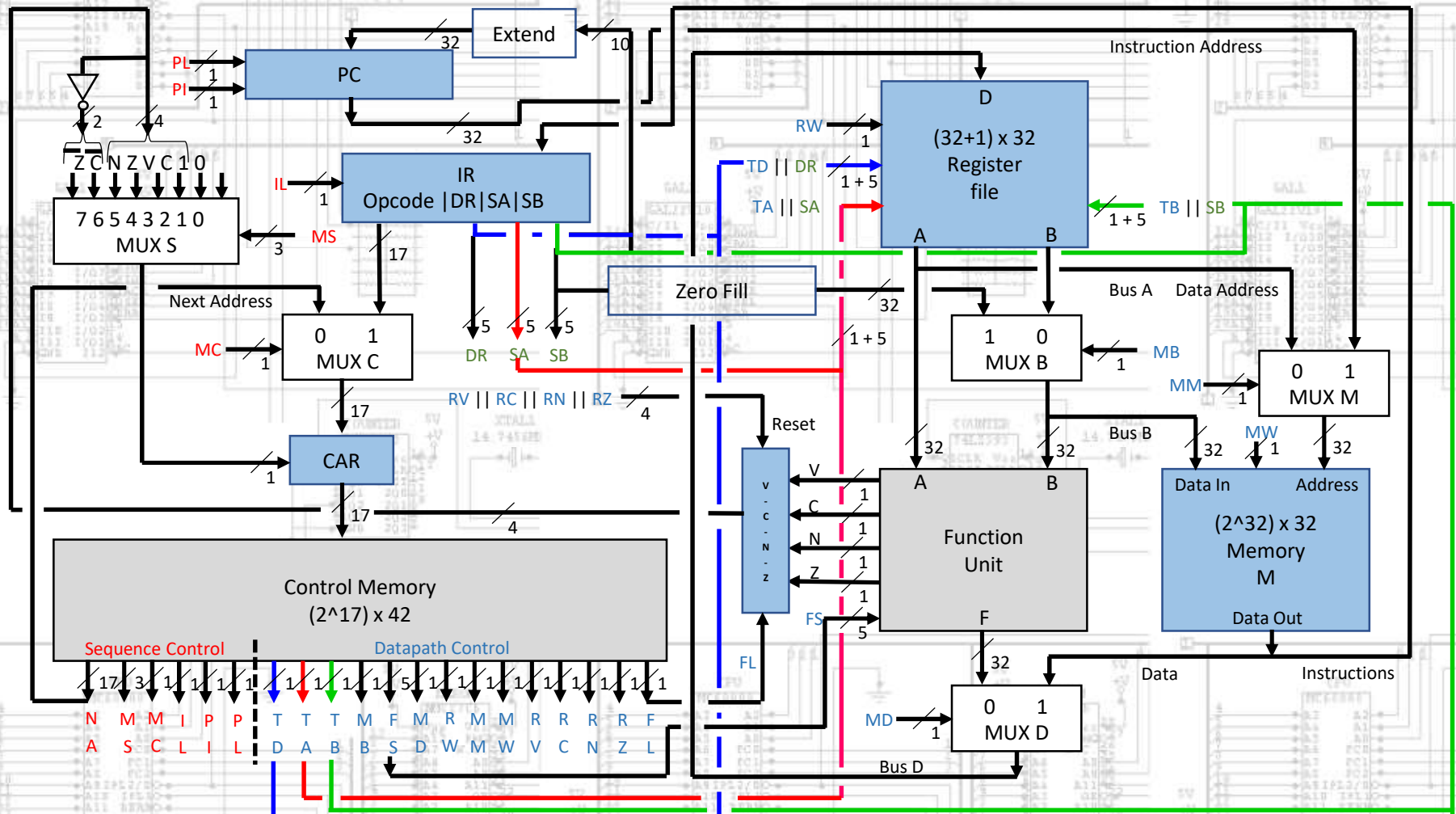

# IR Instruction Register

4	4	3	3	3	3	3	3	3	3	3	3	2	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0	
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0										
Next Address												MS	M	I	P	P	T	T	T	M	FS							M	R	M	M	R	R	R	R	F					
													C	L	I	L	D	A	B	B								D	W	M	W	V	C	N	Z	L					


- ▶ Instructions must be held in a register during the execution of multiple micro-ops
- ▶ The **IR** is only loaded if an instruction is fetched from memory **M**
  - ▶ The **IR** has a load enable control signal **IL**
  - ▶ This signal is part of the control word

# PC Program Counter Register

4	4	3	3	3	3	3	3	3	3	3	3	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0	
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0										
Next Address												MS		M	I	P	P	T	T	T	M	FS				M	R	M	M	R	R	R	R	F							
														C	L	I	L	D	A	B	B					D	W	M	W	V	C	N	Z	L							


- ▶ The PC only increments if an instruction is fetched from memory M
- ▶ The control word has two bits that determine the PC modifications:
  - ▶ PI - increment enable signal
    - ▶  $PC \leftarrow PC + 1$
  - ▶ PL – PC load signal
    - ▶  $PC \leftarrow PC + se\ AD$

# IR - IL; PC - PI - PL

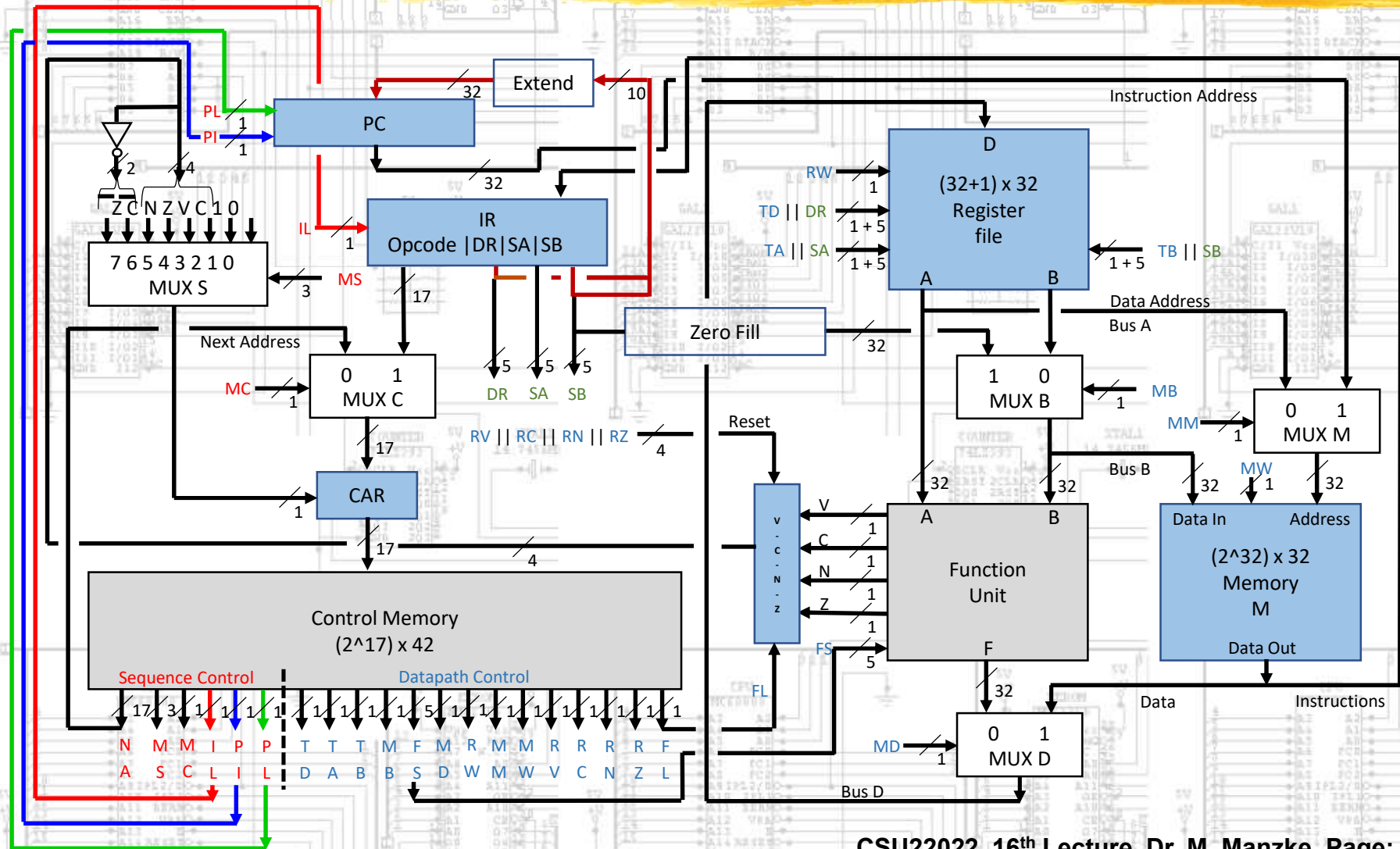




# Next Address Logic

 


- ▶ The **CAR** Control Address Register selects the control word in the 256 x 42 control memory
- ▶ The next logic (**MUX S**) determines whether **CAR** is incremented on loaded.
  - ▶ Controlled with **MS**
- ▶ The source (Opcode or NA) of the loaded address is determined by **MUX C**
  - ▶ Selected by **MC**

# Next Address Field

 


- ▶ The sources for the multiplexer can be:
  - ▶ Contents of the 17 bit **NA** Next Address field
  - ▶ 17 bit from the opcode field in the **IR**
- ▶ An opcode loaded into the **CAR** points to:
  - ▶ Microprogram in Control Memory
  - ▶ This program implements the instruction through the execution of a sequence of micro-operations
- ▶ MUX S determines whether the **CAR** is:
  - ▶ Incremented
  - ▶ Loaded

# Sequencer Control Fields

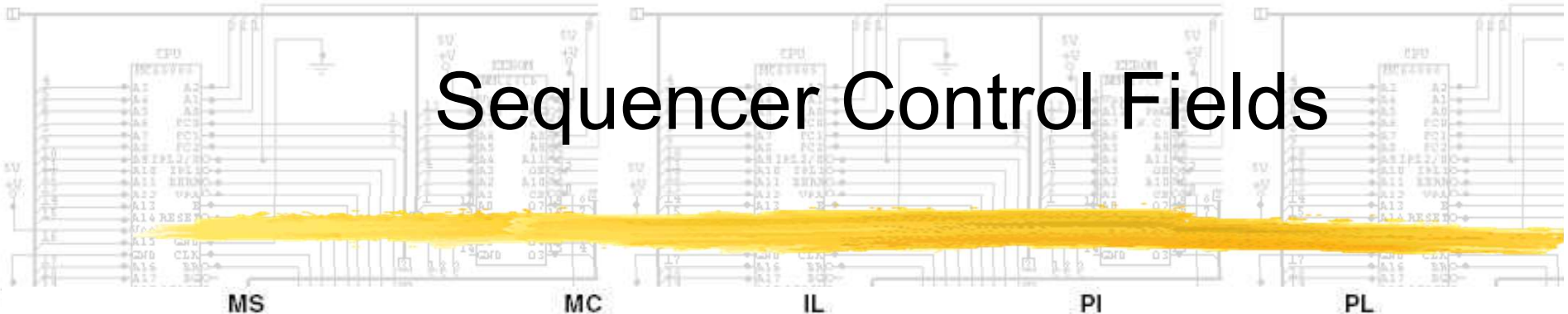

Action	Symbolic Notation	Code	Select	Symbolic Notation	Action	Symbolic Notation	Action	Symbolic Notation	Action	Symbolic Notation	Code
Increment <i>CAR</i>	CNT	000	NA	NXA	No load	NLI	No load	NLP	No load	NLP	0
Load <i>CAR</i>	NXT	001	Opcode	OPC	Load instr.	LDI	Increment PC	INP	Load PC	LDP	1
If <i>C</i> = 1, load <i>CAR</i> ; else increment <i>CAR</i>	BC	010									
If <i>V</i> = 1, load <i>CAR</i> ; else increment <i>CAR</i>	BV	011									
If <i>Z</i> = 1, load <i>CAR</i> ; else increment <i>CAR</i>	BZ	100									
If <i>N</i> = 1, load <i>CAR</i> ; else increment <i>CAR</i>	BN	101									
If <i>C</i> = 0, load <i>CAR</i> ; else increment <i>CAR</i>	BNC	110									
If <i>Z</i> = 0, load <i>CAR</i> ; else increment <i>CAR</i>	BNZ	111									


# NA - MS - MC

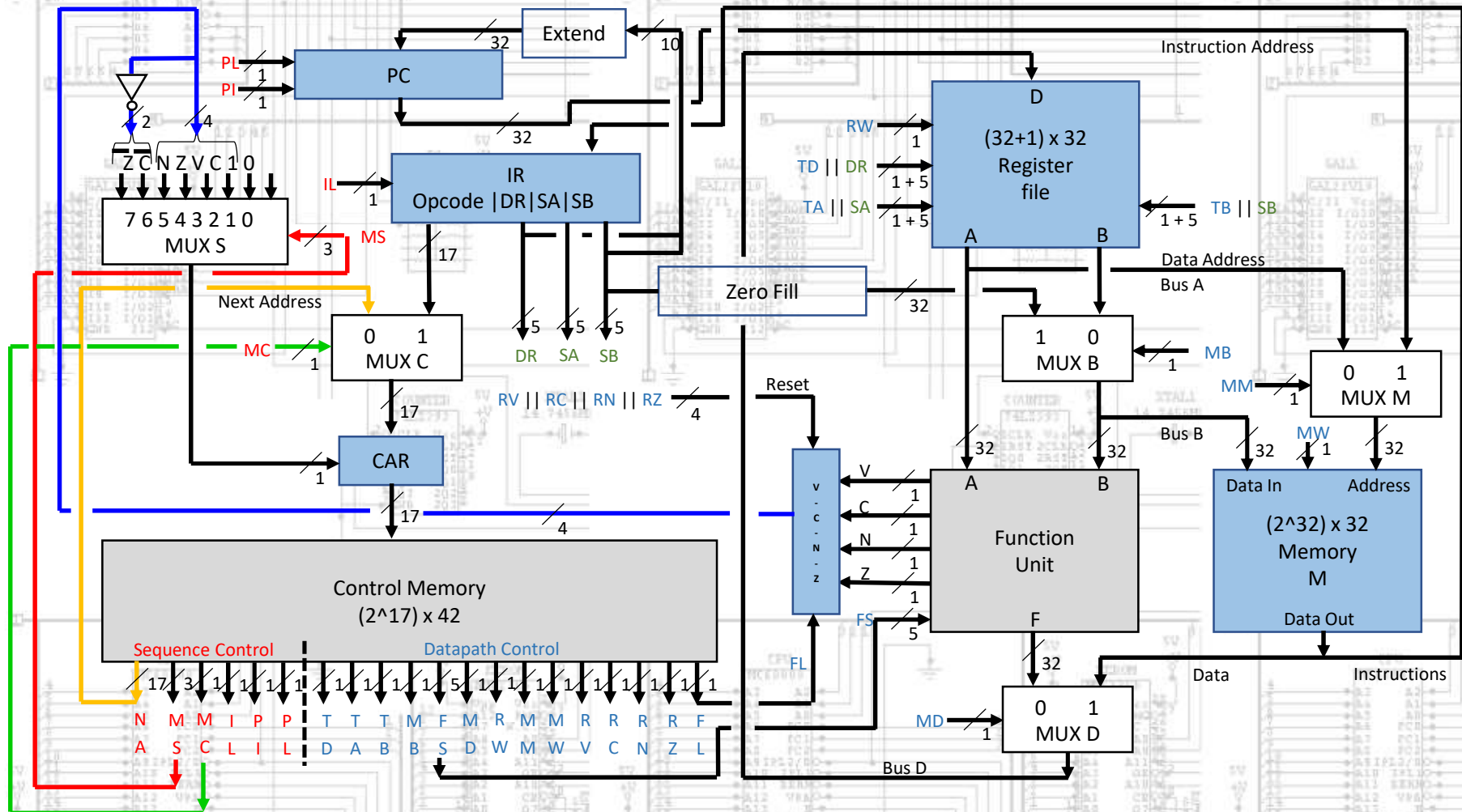



# Microprogram ASM

$C1_{16}$

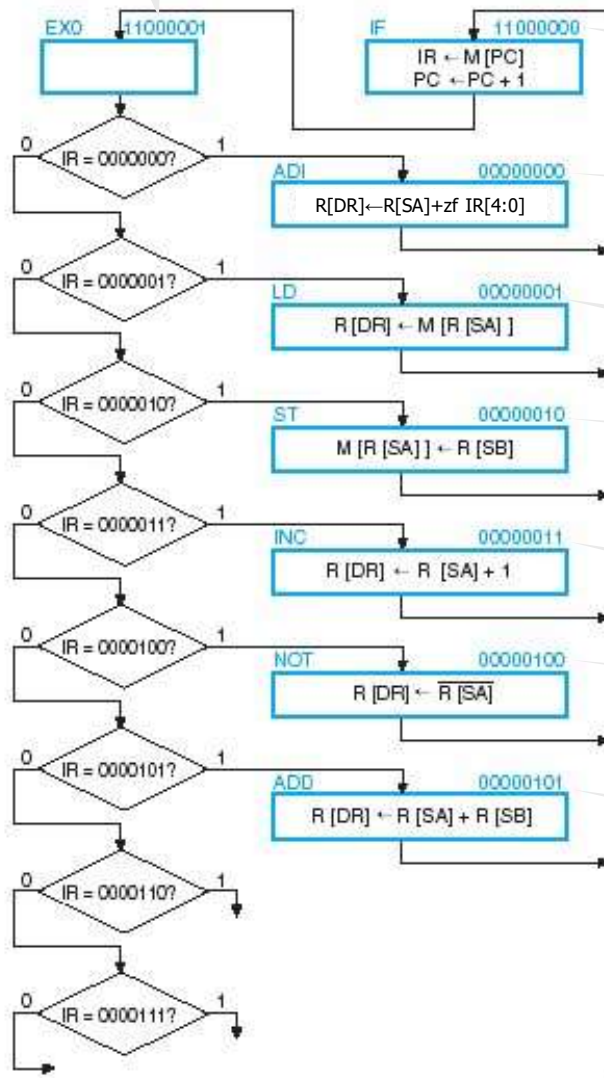

$C0_{16}$

$00_{16}$

$01_{16}$

$02_{16}$

$03_{16}$

$04_{16}$

$05_{16}$

Implementation on page 14

# Microprogram in Control Memory

? = 0<sub>2</sub> or ? = 1<sub>2</sub>

```
-- |41      25|2422|21|20|19|18|17|16|15|14|13  9|8|7|6|5|4|3|2|1|0|
-- | Next Address | MS | M| I| P| P| T| T| T| M| FS |M|R|M|M|R|R|R|F|
-- | Next Address | MS | C| L| I| L| D| A| B| B| FS |D|W|M|W|V|C|N|Z|L|

-- ADI      R[DR]←R[SA]+zf IR[4:0]
"00000000???????? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ",-- 00
-- LD      R[DR]←M[R[SA]]
"00000000???????? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ",-- 01
-- ST      M[R[SA]]←R[SB]
"00000000???????? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ",-- 02
-- INC      R[DR]←R[SA]+1
"00000000???????? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ",-- 03
-- NOT      R[DR]←NOT[R[SA]]
"00000000???????? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ",-- 04
-- ADD      R[DR]←R[SA]+R[SB]
"00000000???????? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ",-- 05
      :
      :
-- IF      IR←M[PC], PC←PC+1
"00000000???????? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ",-- C0
-- EX0     CAR←IR[31:15]
"00000000???????? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ? ",-- C1
```

variable addr : integer;

variable control\_out : std\_logic\_vector(41 downto 0);