

Concurrent Signal Assignment Statements (CSAs)

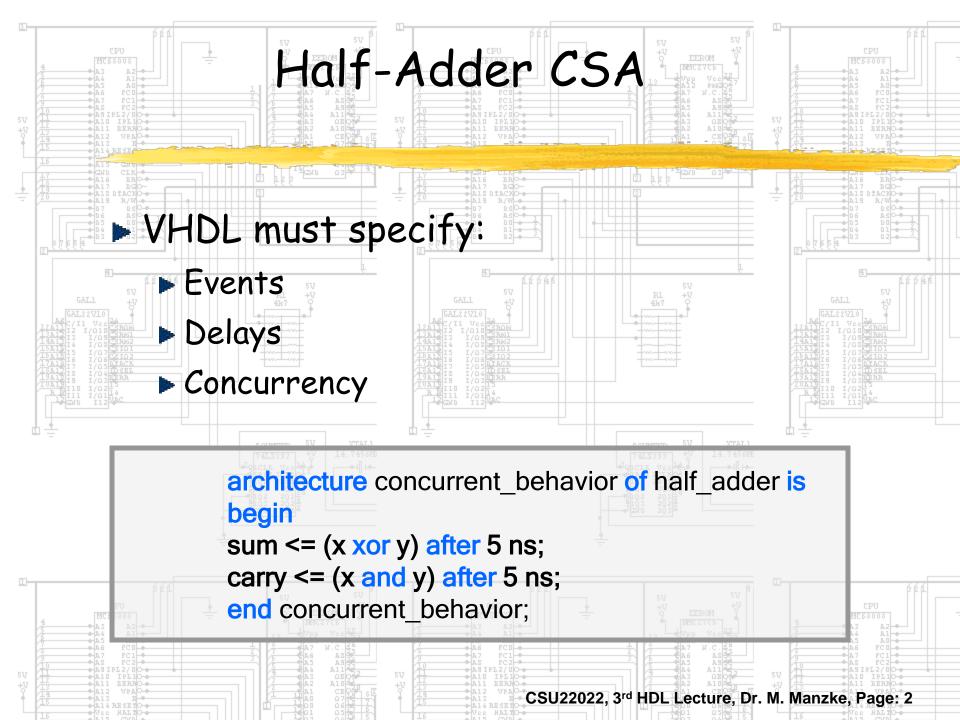- Digital systems operate with concurrent signals
- ► Signals are assigned values at a specific point in time.
- VHDL uses signal assignment statements
 - ► Specify value and time
- Multiple signal assignment statements are executed concurrently
 - ► Concurrent Signal Assignment Statements (CSAs)



CSA Statements

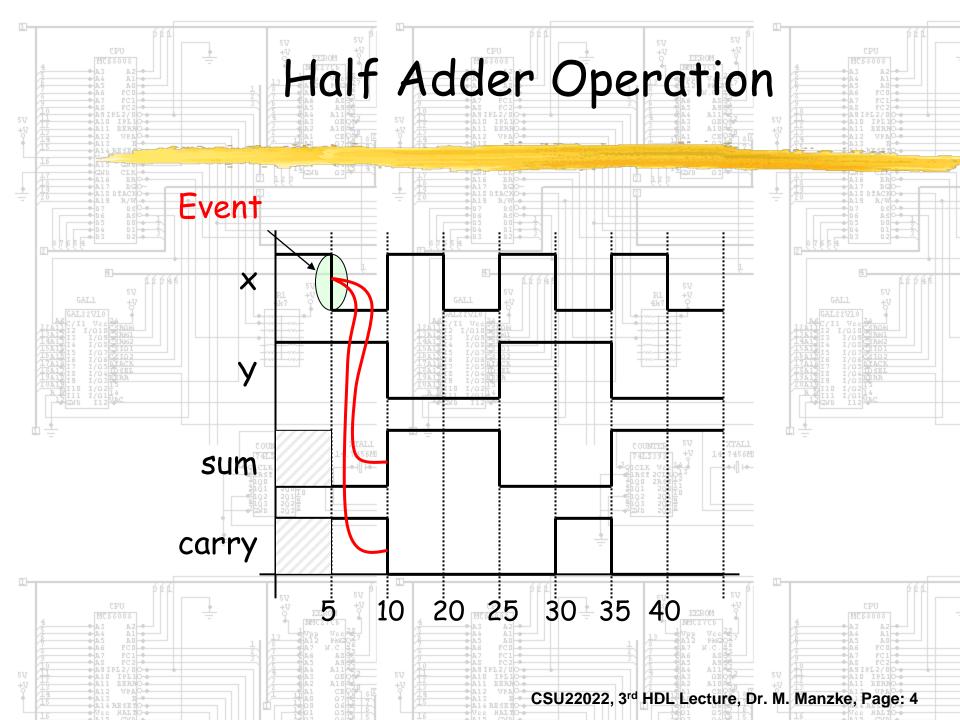- concurrent behavior
 - ► Name of architecture that defines the half_adder entity.
- signal assignment statements
 - sum <= (x xor y) after 5 ns;
 </p>
 - carry <= (x and y) after 5 ns;</p>
- Signal assignment operator <=</p>
 - ▶ Describes how output signals depend on input signals
- An output signal changes if an input signal has changed.



after Keyword


- Signal propagation of the XOR and AND gates must be taken into account.
 - ▶ Both gates require 5 ns propagation delay
- signal assignment statements define this through the after Keyword.
- ► This keyword specifies when the output signal is set to the result of an evaluation after an input signal transition (event).
- ► The textual order of the assignment statement has no influence on the timing.

library and use clauses

library IEEE; use IEEE.STD_LOGIC_1164.ALL; entity 2BA4 is

- A library contains design entities that be used
- ▶ The library IEEE clause defines the IEEE library.
- ► The library may contain packages.
- ► The above example specifies through the use clause the IEEE.STD_LOGIC_1164.ALL packages.
- This package is required for std_logic type declaration.

Full-Adder VHDL library IEEE; use IEEE.STD_LOGIC_1164.ALL; entity full_adder is Port (in1, in2, c in:in std ulogic; sum, c_out:out std_ulogic); end full adder; architecture dataflow of full adder is signal s1,s2,s3: std ulogic; constant gate_delay: Time := 5 ns; begin s1 <= (ln1 xor ln2) after gate_delay; s2 <= (c_in and s1) after gate_delay; s3 <= (ln1 and ln2) after gate_delay; sum <= (s1 xor c_in) after gate_delay;</pre> c_out <= (s2 or s3) after gate_delay; end dataflow; CSU22022, 3rd HDL Lecture, Dr. M. Manzke, Page: 7

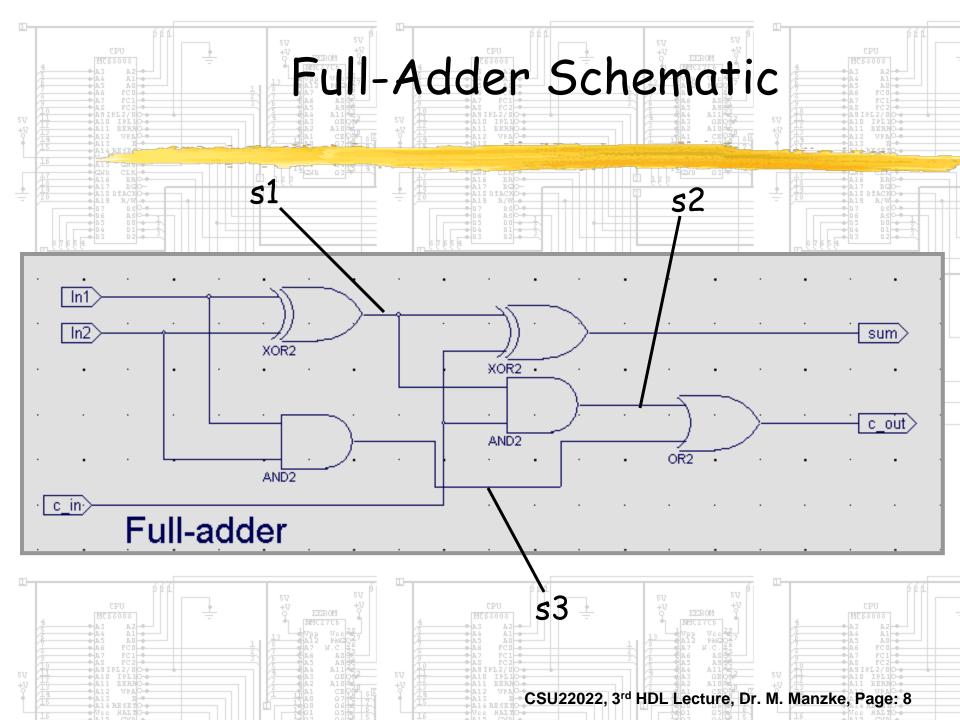

Architecture Declaration

```
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
entity full_adder is
  Port (in1, in2, c in:in std ulogic;
        sum, c_out:out std_ulogic );
end full adder;
architecture dataflow of full adder is
signal s1,s2,s3: std_ulogic;
constant gate_delay: Time := 5ns;
begin
s1 <= (ln1 xor ln2) after gate_delay;
s2 <= (c_in and s1) after gate_delay;
s3 <= (ln1 and ln2) after gate_delay;
sum <= (s1 xor c_in) after gate_delay;</pre>
c_out <= (s2 or s3) after gate_delay;
end dataflow;
```

Architecture Body library IEEE; use IEEE.STD LOGIC 1164.ALL; entity full_adder is Port (in1, in2, c in:in std ulogic; sum, c_out:out std_ulogic); end full adder; architecture dataflow of full adder is signal s1,s2,s3: std ulogic; constant gate_delay: Time := 5ns; begin s1 <= (ln1 xor ln2) after gate_delay; s2 <= (c_in and s1) after gate_delay;</pre> s3 <= (ln1 and ln2) after gate_delay; sum <= (s1 xor c_in) after gate_delay;</pre> c_out <= (s2 or s3) after gate_delay; end dataflow; CSU22022, 3rd HDL Lecture, Dr. M. Manzke, Page: 10

The Full-Adder Model

- The full-adder simulates the signal transitions at gate-level
- The model has three internal signals
- ▶ These signals are not ports to the entity
- The internal signals are declared in the architectural declaration
- ► The Boolean equations define how each signal is derived as function of:
 - Other signals
 - Propagation delay
- Constant can be used to declare a constant of a particular type.
- In this case Time



- Signals are not variables
 - History of values over time
 - Waveform

signal s1: std_ulogic := `0`;

- Signals may use the assignment symbol := followed by an expression
- ▶ The value of the expression will be initial value of the signal
- ▶ If no initialisation is provided the signal receives a default value
- ► VHDL signal types:
 - ▶ Integer, real, bit_vector...

Signals and Time

► A concurrent signal assignment statement (CSA)

sum <= (x xor y) after 5 ns;


- ▶ In a more general form:
 - signal <= value expression after time expression;</p>
- In the example,
 - if x or y change its value the sum will be assigned the result of the (x xor y) evaluation after 5ns.
- The Time-value pair represents the future value of the signal.
 - Also called transaction.

Multiple Signal Transactions

▶ It is possible to specify the following:

 $s1 \le (x \times y)$ after 5 ns, $(x \times y)$ after 10 ns, $(not \times x)$ after 10 ns;

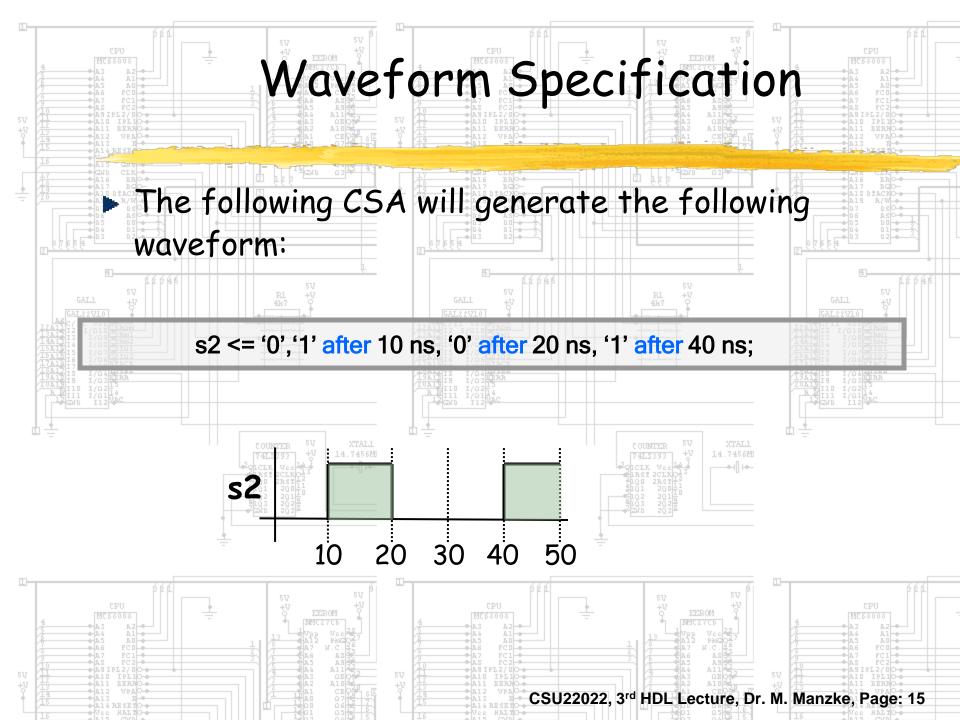- After one of the signals changed all three waveform elements will be evaluated and scheduled according to their after specification.
- ► The simulation keeps an ordered list of all transactions scheduled for a particular signal.
- ▶ The scheduled transactions are also known as:
 - Projected output waveform.





- ▶ In a physical system a wire (signal) has a driver.
- This driver determents the waveform.
- Up the now every signal had one driver only
- But real system have shared signals:
 - Buses
 - ► Wired logic
- ▶ VHDL determines the value of the signal with multiple drivers through a resolution function.

Resolved Type Declaration

- A shared signal must be declared as a resoled type.
- The previous examples used unresolved types:

```
std_ulogic_vector (7 downto 0);
std_ulogic;
```

► The following declaration will make these signal types resolved:

```
std_logic_vector (7 downto 0);
```