
 


Hierarchical VHDL

4-Bit Ripple Carry Adder

 

Hierarchical VHDL (Page 1)

4-Bit Ripple Carry Adder

```
-- 4-bit Adder: Hierarchical Dataflow/Structural
library ieee;
use ieee.std_logic_1164.all;
entity half_adder is
    port (x, y : in std_logic;
          s, c : out std_logic);
end half_adder;

architecture dataflow_3 of half_adder is
begin
    s <= x xor y;
    c <= x and y;
end dataflow_3;
```

Hierarchical VHDL (Page 2)

4-Bit Ripple Carry Adder

```
library ieee;  
use ieee.std_logic_1164.all;  
entity full_adder is  
    port (x, y, z : in std_logic;  
          s, c : out std_logic);  
end full_adder;
```

Hierarchical VHDL (Page 3)

4-Bit Ripple Carry Adder

```
architecture struc_dataflow_3 of full_adder is
  component half_adder
    port(x, y : in std_logic;
          s, c : out std_logic);
  end component;
  signal hs, hc, tc: std_logic;
begin
  HA1: half_adder
    port map (x, y, hs, hc);
  HA2: half_adder
    port map (hs, z, s, tc);
  c <= tc or hc;
end struc_dataflow_3;
```

Hierarchical VHDL (Page 4)

4-Bit Ripple Carry Adder

```
library ieee;  
use ieee.std_logic_1164.all;  
entity adder_4 is  
    port(B, A : in std_logic_vector(3 downto 0);  
          C0 : in std_logic;  
          S : out std_logic_vector(3 downto 0);  
          C4: out std_logic);  
end adder_4;
```

Hierarchical VHDL (Page 5)

4-Bit Ripple Carry Adder

```
architecture structural_4 of adder_4 is
  component full_adder
    port(x, y, z : in std_logic;
         s, c : out std_logic);
  end component;
  signal C: std_logic_vector(3 downto 1);
begin
  Bit0: full_adder
    port map (B(0), A(0), C(0), S(0), C(1));
  Bit1: full_adder
    port map (B(1), A(1), C(1), S(1), C(2));
  Bit2: full_adder
    port map (B(2), A(2), C(2), S(2), C(3));
  Bit3: full_adder
    port map (B(3), A(3), C(3), S(3), C4);
end structural_4;
```

4-Bit Full Adder

Behavioral Description

-- 4-bit Adder: Behavioral Description

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity adder_4_b is

port(B, A : in std_logic_vector(3 downto 0);

C0 : in std_logic;

S : out std_logic_vector(3 downto 0);

C4: out std_logic);

end adder_4_b;

architecture behavioral of adder_4_b is

signal sum : std_logic_vector(4 downto 0);

begin

sum <= ('0' & A) + ('0' & B) + ("0000" & C0);

C4 <= sum(4);

S <= sum(3 downto 0);

end behavioral;

Positive Edge-Triggered D Flip-Flop

Process Description (entity)

-- Positive Edge-Triggered D Flip-Flop with Reset:
-- VHDL Process Description

```
library ieee;  
use ieee.std_logic_1164.all;  
entity dff is  
  port(CLK, RESET, D: in std_logic;  
        Q, Q_n: out std_logic);  
end dff;
```


Positive Edge-Triggered D Flip-Flop

Process Description (architecture)

architecture pet_pr of dff is

- Implements positive edge-triggered bit state storage
- with asynchronous reset.

signal state: std_logic;
begin

Q <= state;

Q_n <= not state;

process (CLK, RESET)

begin

if (RESET = '1') then

state <= '0';

else

if (CLK'event and CLK = '1') then

state <= D;

end if;

end if;

end process;

end;