

CSA vs. Conditional Signal Assignment

- ▶ Concurrent Signal Assignment Statements are suitable for describing gate-level circuits.
- ▶ Models for higher level abstraction are difficult to express with Concurrent Signal Assignment Statements.
- ▶ Higher level abstraction models are required for multiplexors, decoders ...
- ▶ VHDL provides **Conditional Signal Assignment** statements for these situations.

4 to 1 - 8bit Multiplexor

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity mux4 is  
    Port (in0, in1, in2, in3: in std_logic_vector (7 downto 0);  
          s0, s1: in std_logic;  
          z: out std_logic_vector (7 downto 0));  
end mux4;
```

```
architecture behavioural of mux4 is  
begin  
    z <= in0 after 5ns when s0 = '0' and s1 = '0' else  
        in1 after 5ns when s0 = '0' and s1 = '1' else  
        in2 after 5ns when s0 = '1' and s1 = '0' else  
        in3 after 5ns when s0 = '1' and s1 = '1' else  
        "00000000" after 5ns;  
end behavioural;
```


Conditional Signal Assignment

- ▶ In the 4to1 - 8bit multiplexor example:
- ▶ If S1 or S2 changes the concurrent assignment statement is executed.
 - ▶ All four conditions may be checked.
- ▶ The order is relevant.
 - ▶ The evaluation takes place in the order that they appear.
 - ▶ The first true condition determines the output.
 - ▶ The order should reflect the physical implementation.

Waveform (4 to 1 - 8bit Multiplexor)

wave - default

 File Edit Cursor Zoom Bookmark Format Window



0 ps to 708273 ps

4 to 2 - Priority Encoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity four_to_two_priority is
    Port ( S0, S1, S2, S3 : in std_logic;
          Z : out std_logic_vector(1 downto 0));
end four_to_two_priority;

architecture Behavioral of four_to_two_priority is
begin
    Z <= "00" after 5 ns when S0='1' else
        "01" after 5 ns when S1='1' else
        "10" after 5 ns when S2='1' else
        "11" after 5 ns when S3='1' else
        "00" after 5 ns;
end Behavioral;
```


Conditional Signal Assignment

▶ The order in the conditional signal assignment statement in the 4 to 2- Priority Encoder example is important.

▶ Note in the example:

- ▶ The last statement set the output to zero.
- ▶ This is necessary because the select signals can have values other than '1' and '0'.
- ▶ This is the case because the select signals are declared as `std_logic` and `std_logic_vector`.

Waveform (4 to 2 -Priority Encoder)

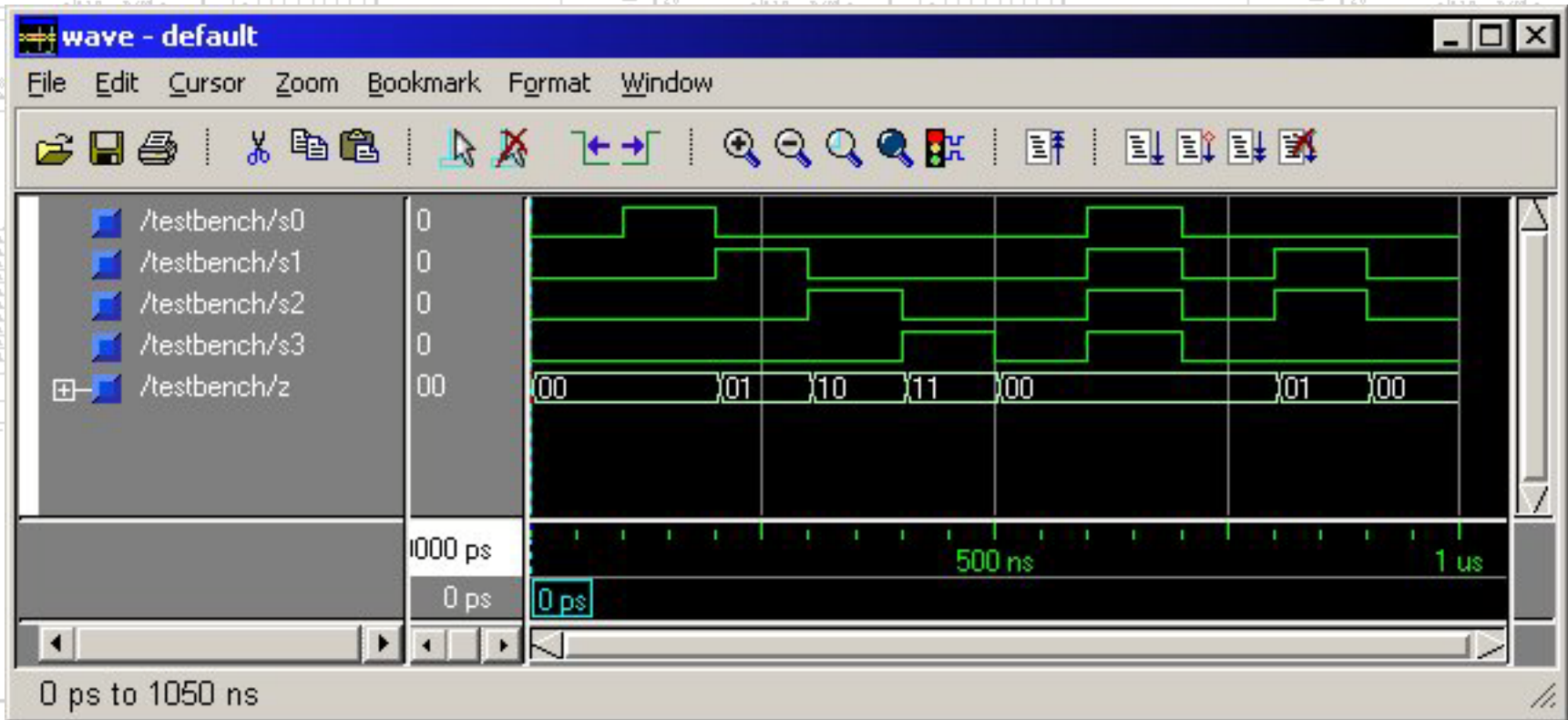


Unaffected

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity four_to_two_priority is
    Port ( S0, S1, S2, S3 : in std_logic;
          Z : out std_logic_vector(1 downto 0));
end four_to_two_priority;

architecture Behavioral of four_to_two_priority is
begin
    Z <= "00" after 5 ns when S0='1' else
        "01" after 5 ns when S1='1' else
        unaffected when S2='1' else
        "11" after 5 ns when S3='1' else
        "00" after 5 ns;
end Behavioral;
```


Waveform (Unaffected)

 

Selected Signal Assignment Statement


- ▶ Signal value is determined by the select expression
- ▶ In this example we read from a register file with eight registers (reg0...reg7)
 - ▶ Read only register file with two read ports

%000	\$12345678	reg0
%001	\$ABCDEF00	reg1
%010	\$12345678	reg2
%011	\$ABCDEF00	reg3
%100	\$12345678	reg4
%101	\$ABCDEF00	reg5
%110	\$12345678	reg6
%111	\$ABCDEF00	reg7

SSA Statement Example

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity reg_file is
    Port ( addr1, addr2 : in std_logic_vector(2 downto 0);
          reg_out_1, reg_out_2 : out std_logic_vector(31 downto 0));
end reg_file;
architecture Behavioral of reg_file is
    signal reg0, reg2, reg4, reg6: std_logic_vector(31 downto 0):= x"12345678";
    signal reg1, reg3, reg5, reg7: std_logic_vector(31 downto 0):= x"abcdef00";
    begin
        with addr1 select
            reg_out_1 <= reg0 after 5 ns when "000",
                      reg1 after 5 ns when "001",
                      reg2 after 5 ns when "010",
                      reg3 after 5 ns when "011",
                      reg3 after 5 ns when others;
        with addr2 (1 downto 0) select
            reg_out_2 <= reg0 after 5 ns when "00",
                      reg1 after 5 ns when "01",
                      reg2 after 5 ns when "10",
                      reg3 after 5 ns when "11",
                      reg3 after 5 ns when others;
    end Behavioral;
```

Waveform (Select)

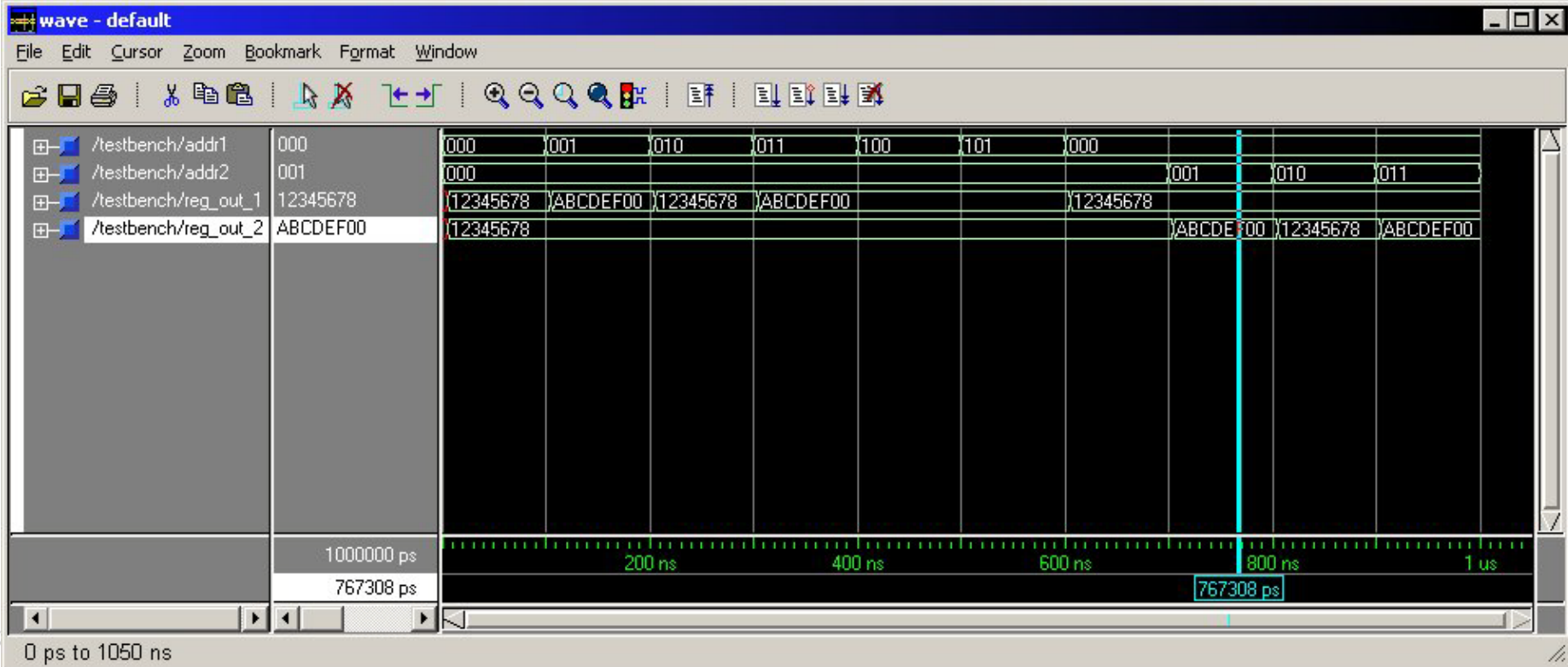

Selected Signal Assignment

- ▶ Similar to case statement in conventional languages.
- ▶ Choices are not evaluated in sequence.
- ▶ Only one must be true.
- ▶ The statement must cover all possible combinations.
- ▶ The **others** clause must be used in situation where not all possible combinations are covered by the select statement.

reg3 after 5 ns when others;

- ▶ In the second select statement operates on a subset of the address range (addr2 (1 **downto** 0)).
- ▶ The **when others** clause is still required because addr2 is declared as **std_logic_vector** and can therefore take 9 values.
- ▶ **unaffected** is may also be used in this type of statement.

```
with addr2 (1 downto 0) select  
  reg_out_2 <= reg0 after 5 ns when "00",  
  reg1 after 5 ns when "01",  
  reg2 after 5 ns when "10",  
  reg3 after 5 ns when "11",  
  reg3 after 5 ns when others;  
end Behavioral;
```