

Bus-based Transfers

- ▶ Digital systems typically have a considerable number of registers N .
- ▶ Typically $8 \leq N \leq 256$
- ▶ Programmer need to be able to make transfers between any pair of them.
- ▶ Let us consider the $N=3$ and use 2:1 MUXs to interconnect $R0, R1, R2$.
- ▶ The result is on the next slide.

Register Transfer via MUX Diagram

The diagram illustrates a register transfer mechanism using three 2-to-1 multiplexers (MUX) and three registers (R0, R1, R2). Each MUX has two data inputs (0 and 1) and a select input (S). The select inputs are labeled "Select S0S1S2". The outputs of the MUXes are connected to the "Load" inputs of the registers, labeled "Load LOL1L2". The registers are represented by blue rectangles. The diagram is set against a background of a complex circuit board with various components like CPUs, GALs, and counters.

CSU22022, 4th Lecture, Dr. M. Manzke, Page: 2


Register Transfer via MUXs

- ▶ This is a very flexible system for it can make up to three independent transfers in one clock period.

RT	S2 S1 S0	L2 L1 L0	Description
$R2 \leftarrow R1$	1 X X	1 0 0	Point-to-Point
$R2 \leftarrow R1, R1 \leftarrow R2$	1 1 X	1 1 0	Reg. Exchange
$R2 \leftarrow R1, R1 \leftarrow R0$ $R0 \leftarrow R2$	1 0 0	1 1 1	Reg. Rotate
$R2 \leftarrow R0, R1 \leftarrow R0$	0 0 X	1 1 0	Reg. broadcast

- ▶ But this is very costly in terms of interconnect, requiring $6 \cdot n$ MUX input connections.
- ▶ To connect $N \cdot n$ -bit registers will require $(N-1) \cdot N \cdot n$ wires.

Register Transfer via MUX & Bus

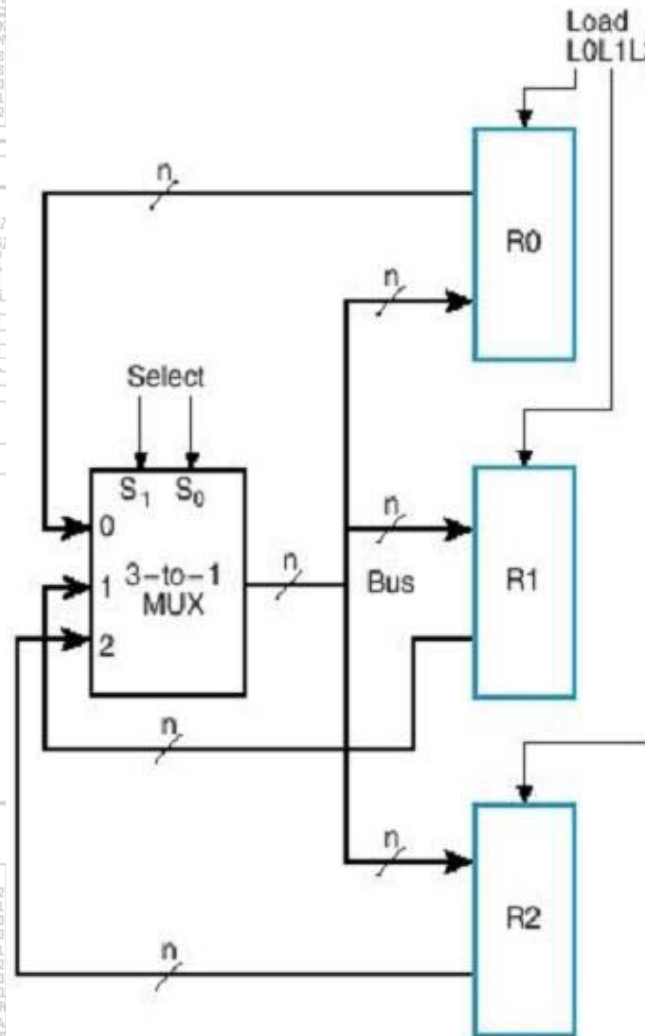

To reduce the amount of interconnects we can use 3-1 MUXs with a single MUX-to-Register bus connection.

Register Transfer via 3-1 MUXs and MUX-to-Register Bus




- ▶ This results in the loss of some flexibility:

RT	S1 S0	L2 L1 L0	Description
$R0 \leftarrow R2$	1 0	0 0 1	Point-to-Point
$R0 \leftarrow R1, R2 \leftarrow R1$	0 1	1 0 1	Reg. Broadcast
$R0 \leftarrow R1, R1 \leftarrow R0$	IMPOSSIBLE		Single source only


- ▶ But the MUX input connections have reduced from $6*n$ to $3*n$.
- ▶ For N Register we need only $N*n$ wires.

Tri-state Bus

   - ▶ Tri-state buffers provide the means to construct a wired-or of arbitrary fan-in, with which we can effectively disperse the MUX on the previous slide right back to the register latches. That is we build our 3:1 MUX as:



Tri-state-bus vs. MUX-bus

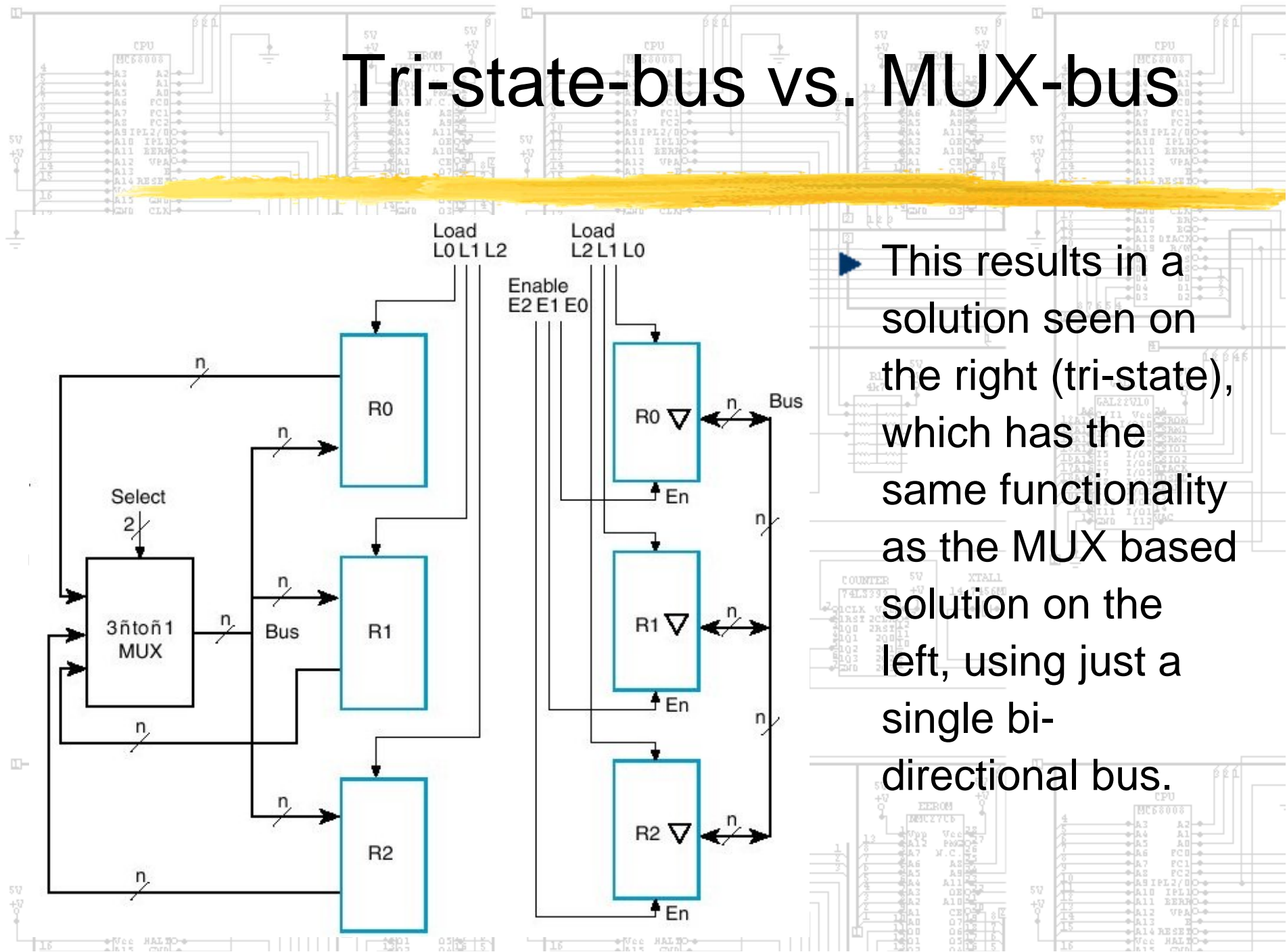

- ▶ This results in a solution seen on the right (tri-state), which has the same functionality as the MUX based solution on the left, using just a single bi-directional bus.

Bi-directional Tri-state Bus

RT	E2 E1 E0	L2 L1 L0	Description
$R0 \leftarrow R2$	1 0 0	0 0 1	Point-to-Point
$R0 \leftarrow R1, R2 \leftarrow R1$	0 1 0	1 0 1	Reg. Broadcast
$R0 \leftarrow R1, R1 \leftarrow R0$	IMPOSSIBLE		Single source only


- With this arrangement it is possible to connect $N \times n$ -bit register with $N-1$ paths of width n .

Memory Transfers

- ▶ Typically processor memories are addressed by a number of address registers:
 - ▶ **PC, MAR, IOR**
- ▶ Address register information is transmitted over an address bus to memory **M**.
- ▶ Similarly data is transferred to/from a number of data registers over a data bus.
 - ▶ **Data register: IR, DR, BUF**
- ▶ The schematic on the next slide illustrates how we may organise three address register **A**, selected by **I**, and data register **D**, selected by **J**, to implement read/write on memory **M**.

READ:
WRITE:

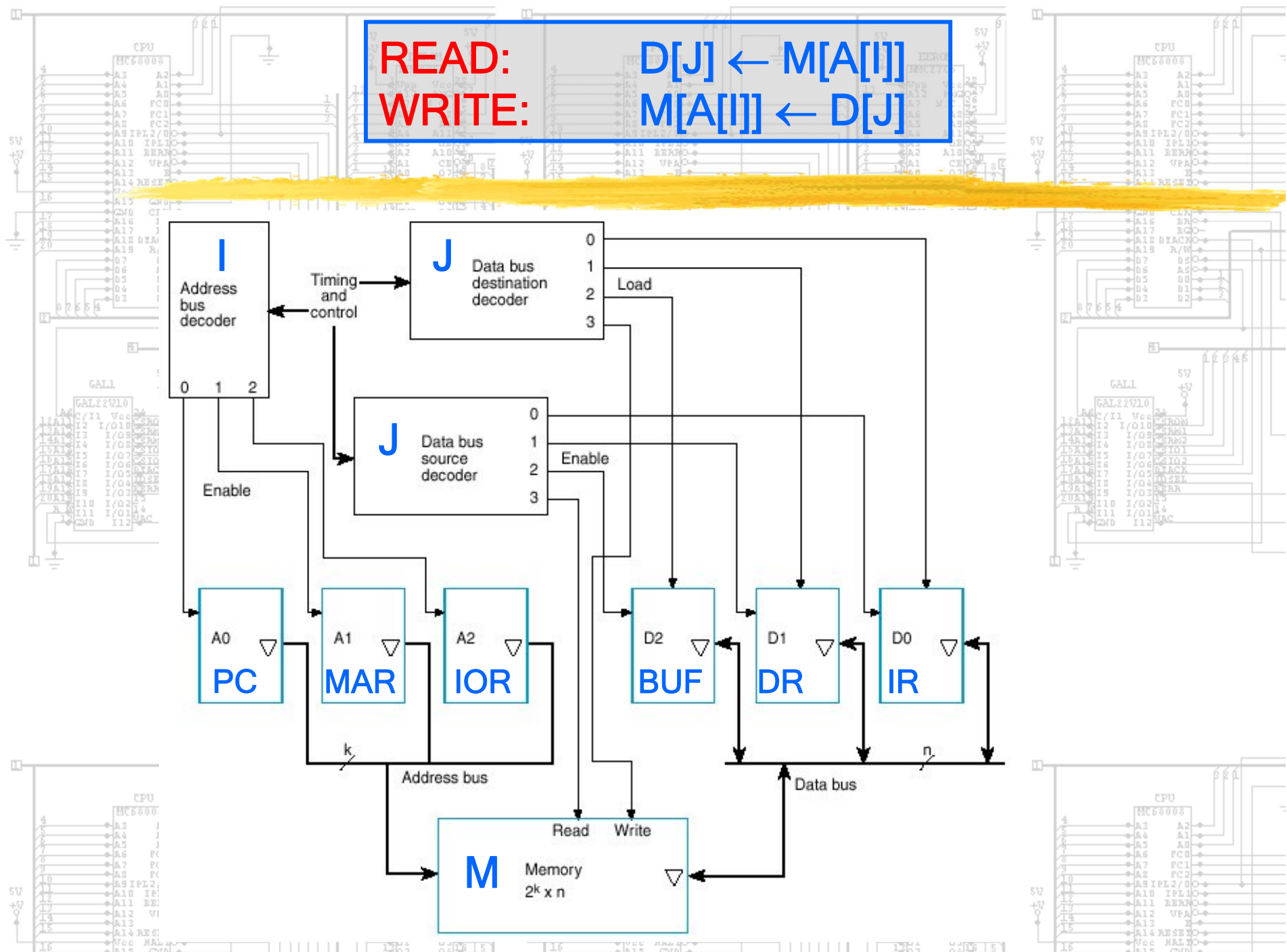$D[J] \leftarrow M[A[I]]$
 $M[A[I]] \leftarrow D[J]$



Datapath

▶ In all digital systems we can partition the structure into two sections:

- The data path which performs data-processing operations on the data stream.
- The control unit which determines the schedule for these data processing operations.

Control Inputs

Control Unit

Control Outputs

Control Signals


Status Signals

Data Input

Datapath

Data Output

Datapath Schematic

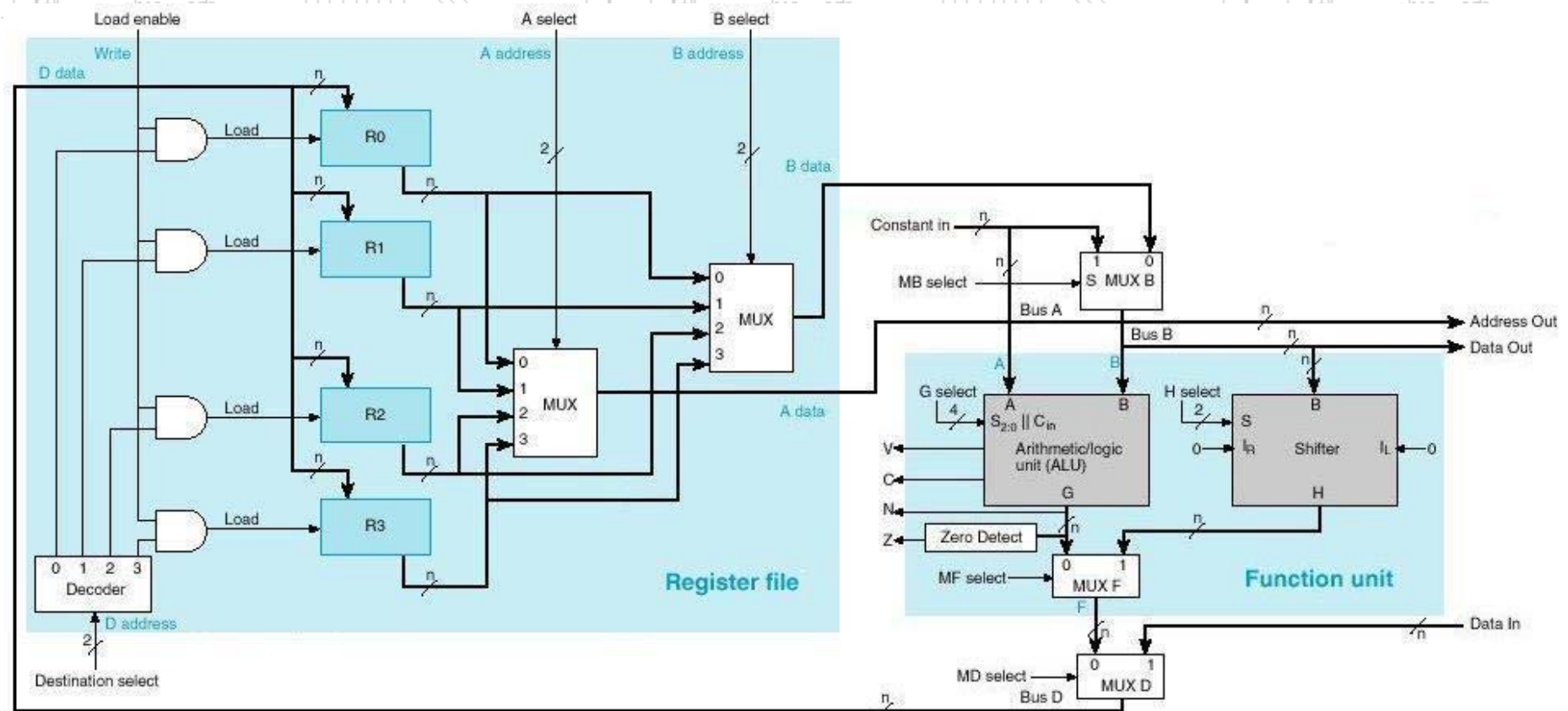

Register File & Functional Unit

- ▶ In practice the three functional micro-ops are implemented in one compact circuit, the **Function Unit**, composed of the **ALU** and **Shifter**.
- ▶ Data for this **Function Unit** comes from a physical adjacent **Register file**, with dual MUX-busses able to supply two operands per clock cycle.
- ▶ Since the register file is itself modest in size typically 8-32 register, there must be provision to send and receive data to/from the main memory system via **DATA IN** and **DATA OUT**.