

# Microprogrammed Control

▶ Hardwired control units have the advantage of great compactness and low propagation delay on account of the shorter loop path.

▶ However as the number of states and control signals increases they become increasingly costly to:

▶ Design

▶ Debug

▶ Upgrade

▶ A more flexible approach is used.

# The Flexible Approach

▶ We store the control words, together with next-state information, in a control memory which is usually:


▶ ROM

▶ EPROM

▶ Then use the control inputs and status signals to select the appropriate address of the next state.

▶ See figure on the next slide.
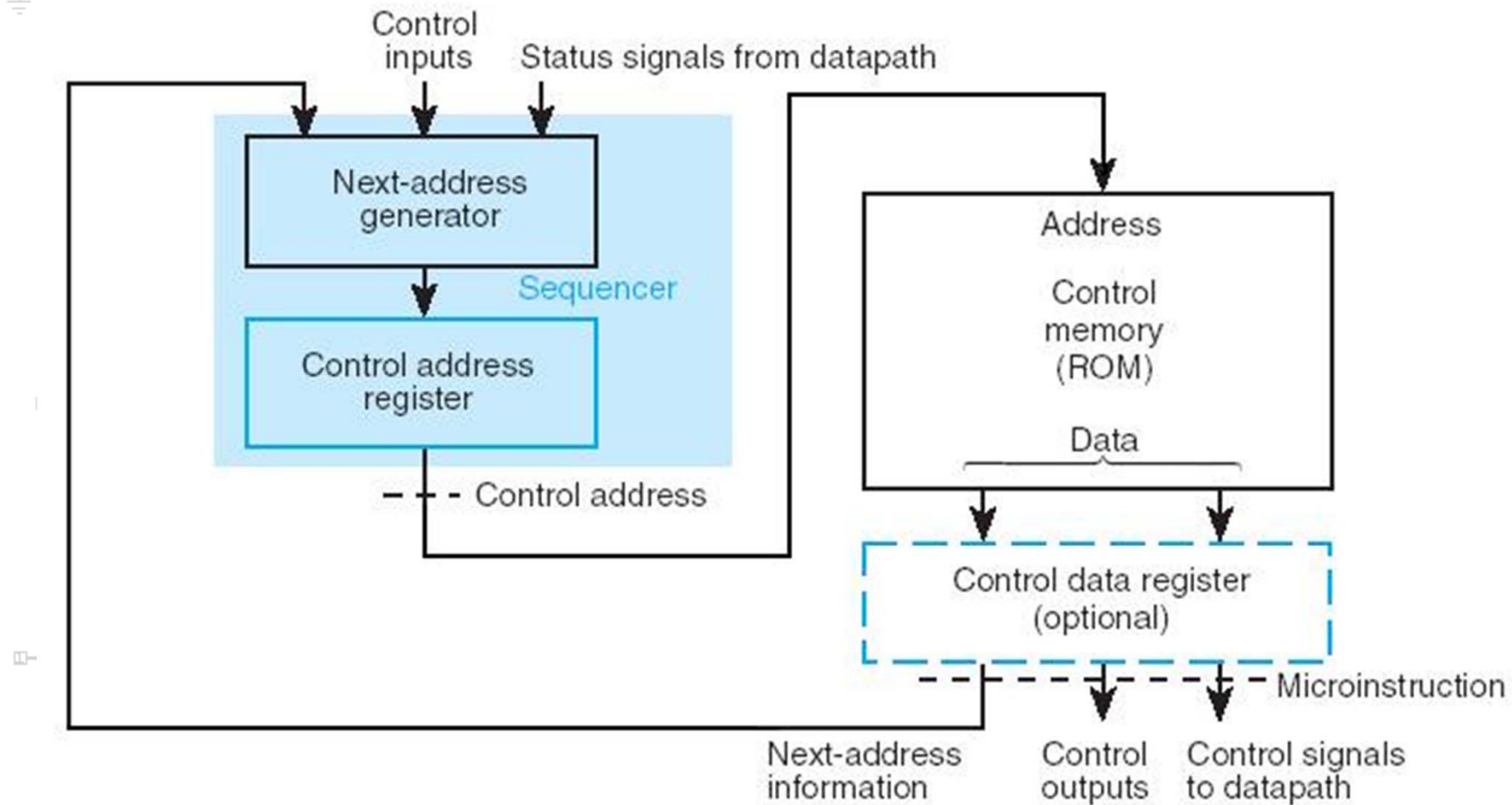
# Microprogrammed Control Unit Organization




# Control Input

▶ One difference which emerges is that since control words are now stored, they cannot be made to depend dynamically on the value of the control input

<u>STATE</u>	<u>Control Input</u>	<u>RT</u>	<u>Control Word</u>
IDLE • $G=0$		none	$CW_1$
IDEL • $G=1$		$C, A \leftarrow 0$	$CW_2$
MULO • $Q_0=0$		none	$CW_3$
MULO • $Q_0=1$		$A \leftarrow A+B, C \leftarrow C_{out}$	$CW_4$
more		more	more




# Binary Multiplier ASM

 

▶ Hence we must introduce additional states to supply these alternative control words.

▶ See next slide
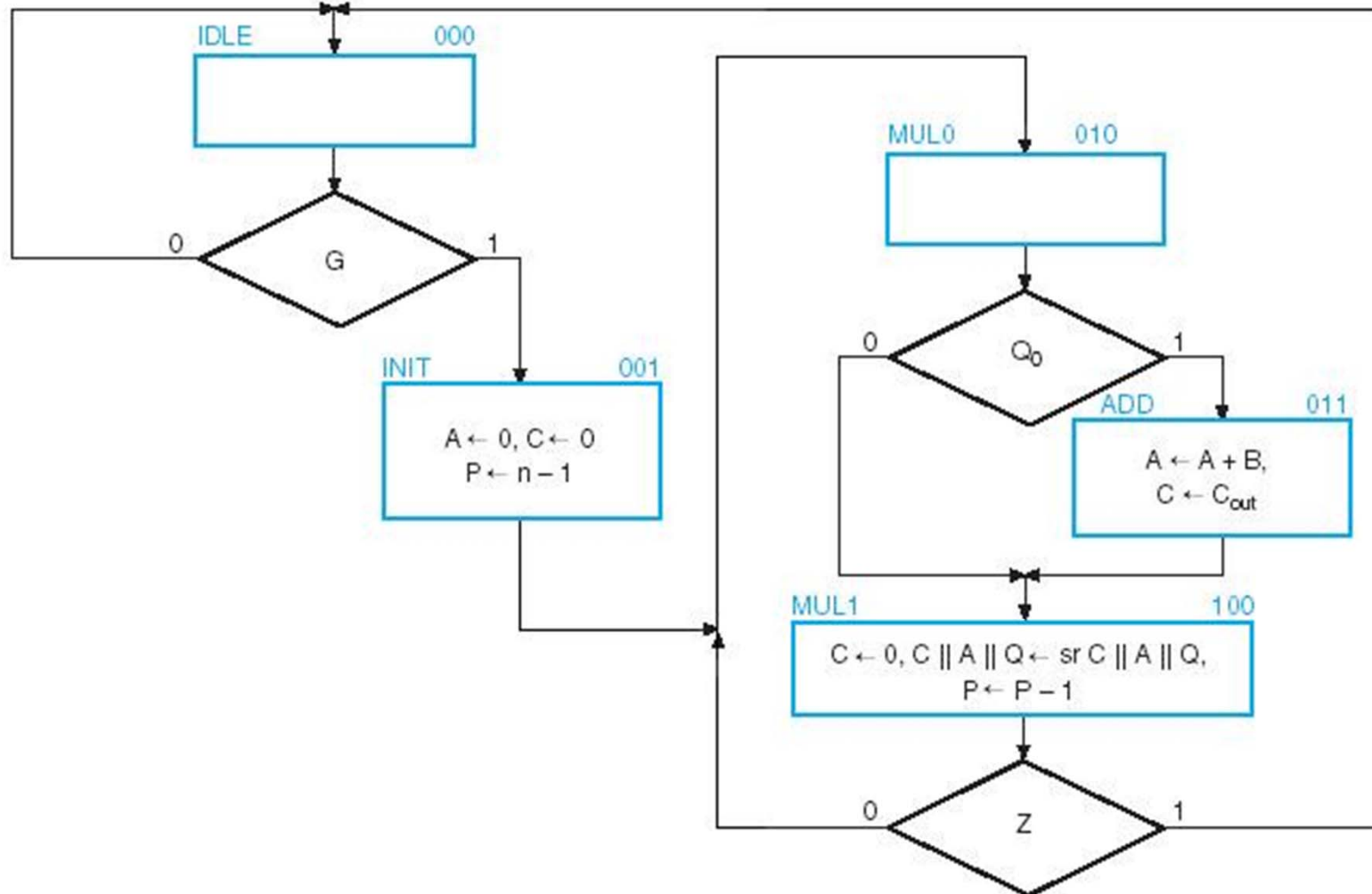
# Microprogrammed Control Unit Binary Multiplier



# Control Address Register (CAR)

► This gives five states so that the control memory must store five control words

► We will need a 3-bit address register

► Control Address Register (CAR)

# SEL bits

► The sequence must be able to respond to two status bits:

► Z  
► Q<sub>0</sub>

► One control input:

► G

► Hence two SEL bits must be included in the control word.



# Next-Address Fields

- ▶ Finally we add two next-address fields:
  - ▶ NXTADD0
  - ▶ NXTADD1
- ▶ This design makes no assumption about the sequence control word accesses.
- ▶ The functional design of the sequence is as follows on the next slide:

# SEL Field Definition

Symbolic notation	Binary Code	Sequencing Microoperations
NXT	00	$CAR \leftarrow NXTADD0$
DG	01	$\overline{G}: CAR \leftarrow NXTADD0$ $G: CAR \leftarrow NXTADD1$
DQ	10	$\overline{Q}_0: CAR \leftarrow NXTADD0$ $Q_0: CAR \leftarrow NXTADD1$
DZ	11	$\overline{Z}: CAR \leftarrow NXTADD0$ $Z: CAR \leftarrow NXTADD1$


# Control Signals for Multiplier control

▶ The control word must supply four control signals:

Control Signal	Register Transfers	States in Which Signal is Active	Micro-instruction Bit Position	Symbolic Notation
Initialize	$A \leftarrow 0, P \leftarrow n - 1$	INIT	0	IT
Load	$A \leftarrow A + B, C \leftarrow C_{out}$	ADD	1	LD
Clear_C	$C \leftarrow 0$	INIT, MUL1	2	CC
Shift_dec	$C \  A \  Q \leftarrow sr C \  A \  Q, P \leftarrow P - 1$	MUL1	3	SD


# Control Word

▶ This results in a 12-bit control word:

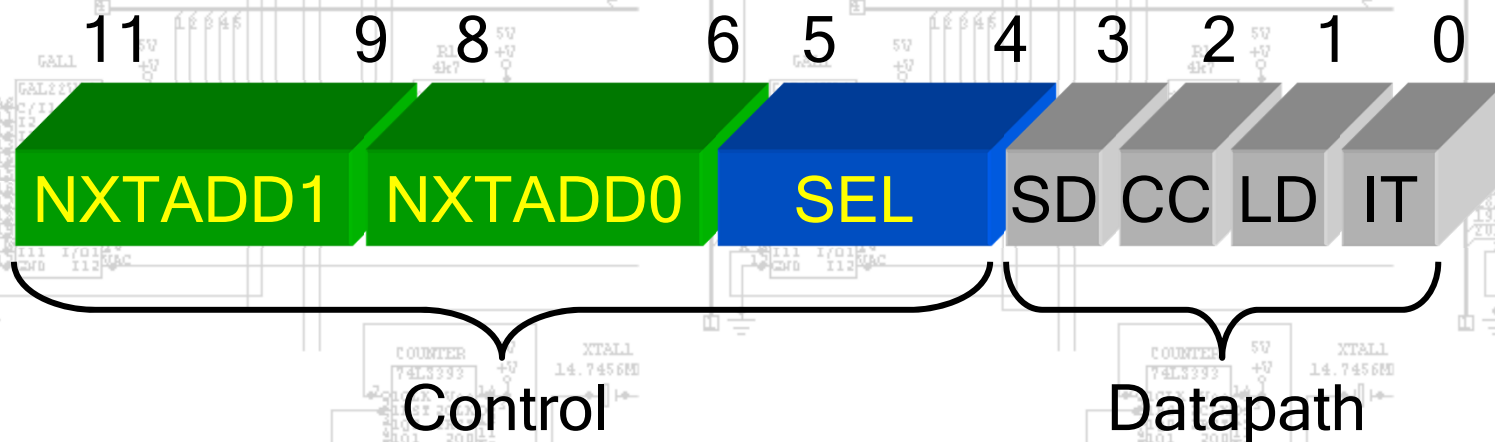



# Control Unit

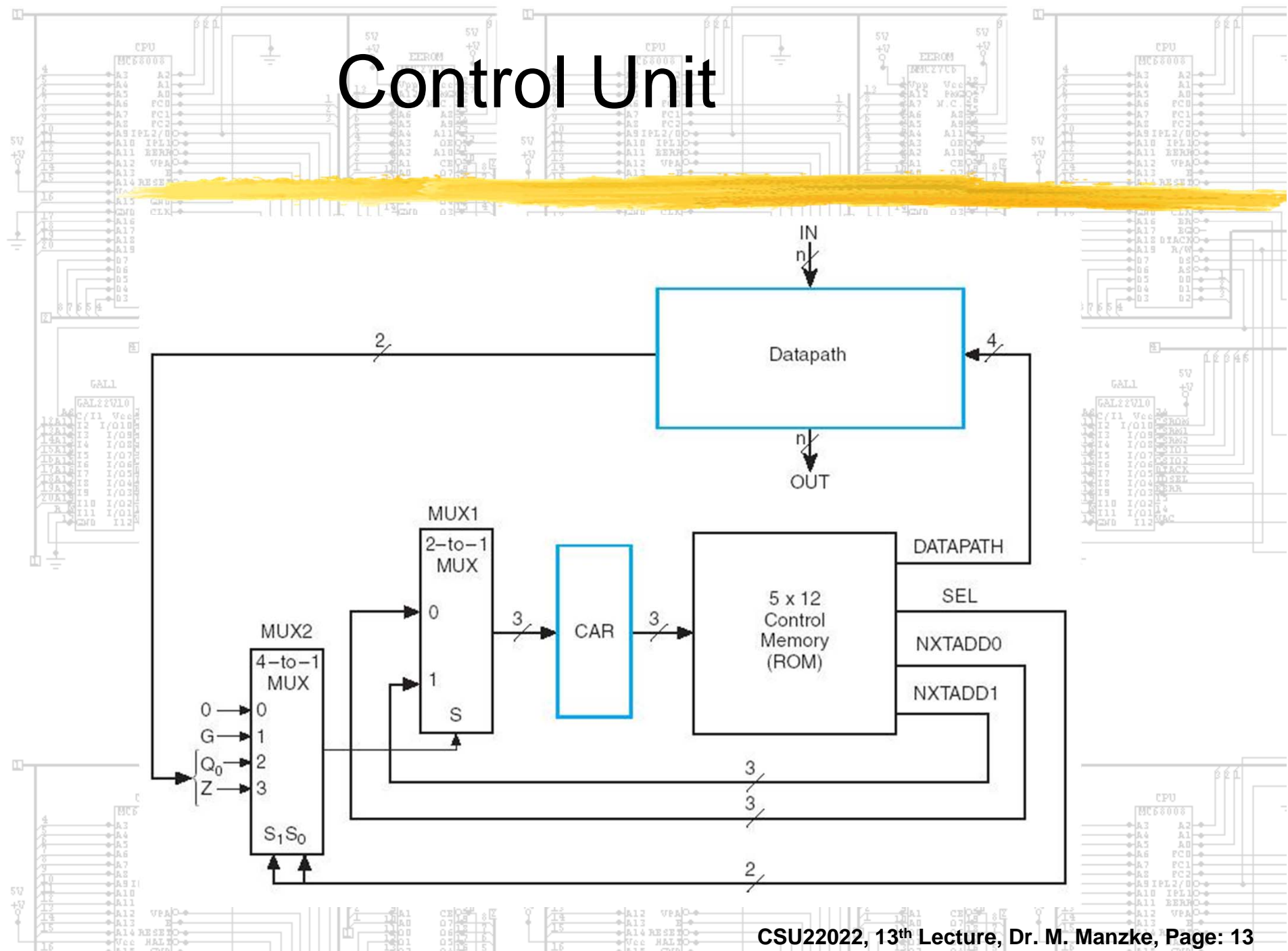

# Register Transfer Description

▶ Next we design the microprogram in symbolic RT form:

Address

Symbolic transfer statement

IDLE

$G: CAR \leftarrow INIT, \bar{G}: CAR \leftarrow IDLE$

INIT

$C \leftarrow 0, A \leftarrow 0, P \leftarrow n-1, CAR \leftarrow MUL0$

MUL0

$Q_0: CAR \leftarrow ADD, \bar{Q}_0: CAR \leftarrow MUL1$

ADD

$A \leftarrow A + B, C \leftarrow C_{out}, CAR \leftarrow MUL1$

MUL1

$C \leftarrow 0, C \| A \| Q \leftarrow sr\ C \| A \| Q, Z: CAR \leftarrow IDLE, \bar{Z}: CAR \leftarrow MUL0, P \leftarrow P-1$

# Symbolic Microprogram & Binary Microprogram

Address	NXTADD1	NXTADD0	SEL	DATAPATH	Address	NXTADD1	NXTADD0	SEL	DATAPATH
IDLE	INIT	IDLE	DG	None	000	001	000	01	0000
INIT	—	MUL0	NXT	IT, CC	001	000	010	00	0101
MUL0	ADD	MUL1	DQ	None	010	011	100	10	0000
ADD	—	MUL1	NXT	LD	011	000	100	00	0010
MUL1	IDLE	MUL0	DZ	CC, SD	100	000	010	11	1100

