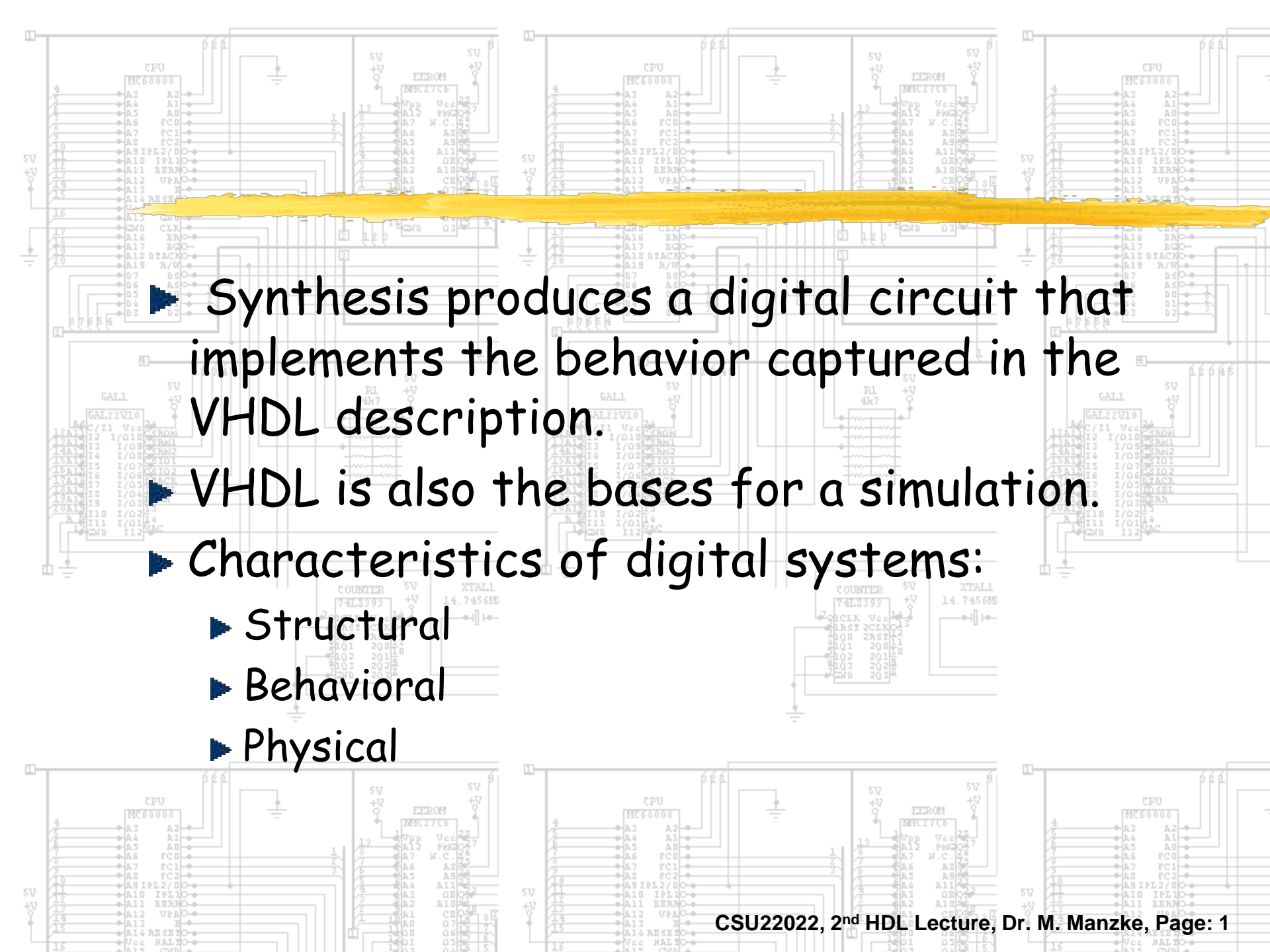


- 
- ▶ Synthesis produces a digital circuit that implements the behavior captured in the VHDL description.
 - ▶ VHDL is also the bases for a simulation.
 - ▶ Characteristics of digital systems:
 - ▶ Structural
 - ▶ Behavioral
 - ▶ Physical

Event, Propagation Delays and Concurrency

Event

Concurrency

Propagation delay

Signals

- ▶ May be 0, 1, or Z
- ▶ Equivalent to wires in digital circuits
- ▶ May be assigned values
- ▶ Signals are associated with time values
- ▶ Sequences of values determines the waveform
- ▶ Signal type depends on the level of abstraction
 - ▶ At gate level through wires (or, and, xor...)
 - ▶ At module level through integer (ALU...)

Shared Signals

► Hardware description languages must be expressive enough to describe signal that may be driven by one or more sources.

► Bus

Design Entity

► Design entities could be:

► Board

► Chip

► Gate

► Transistor

► This design component behavior must be:

► Described


► Simulated

Design Entity -Gate Level Example

► Half-Adder

► Input signals: x, y

► Output signals: sum, carry

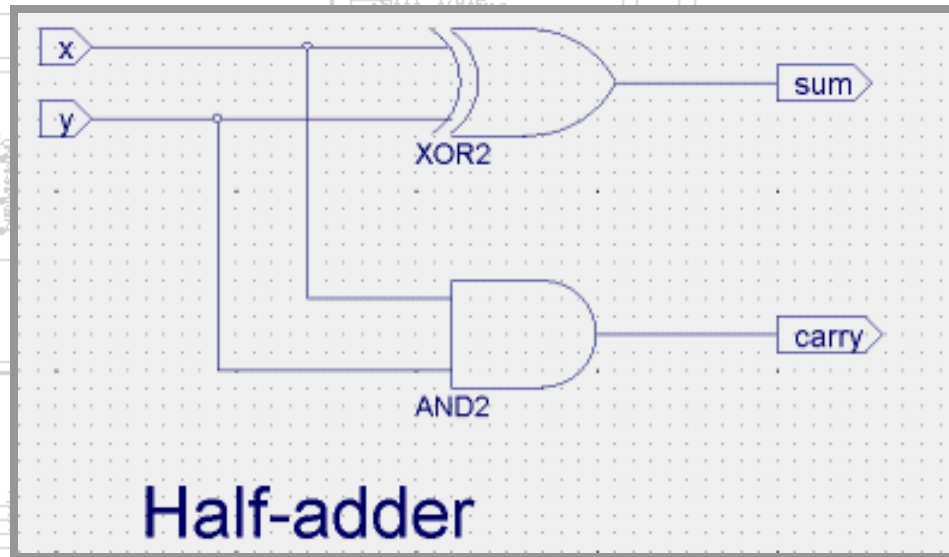

Half-adder

Design Entity - Description

- ▶ Input signals
- ▶ Output signals
- ▶ Behavior
 - ▶ Truth table
 - ▶ Boolean equation
 - ▶ Wires between gates
- ▶ Two components in the design-entity description:
 - ▶ The interface
 - ▶ Internal behavior

Entity Declaration

- ▶ Interface to design entities through
- ▶ Entity Declaration:

Blue = Keywords

Design Entity Name

```
entity half_adder is
  Port ( x : in bit;
         y : in bit;
         sum : out bit;
         carry : out bit);
end half_adder;
```

Port = input & output

Declaration Details

- ▶ **Blue bold** type denotes VHDL reserved keywords (entity, port, ...)
- ▶ VHDL is not case sensitive
 - ▶ Half-adder = HALF-ADDER
- ▶ Ports define the input and output of the the design entity
- ▶ **Ports are signals** that enable communication between the design entity and other entities.
- ▶ Port signals must declare their types.

Port Declaration

- ▶ Signal types defined in the VHDL language

- ▶ **bit**

- ▶ Represents a single-bit signal

- ▶ **bit_vector**

- ▶ Represents a vector of signal of type **bit**

- ▶ Bit and bit_vector are only two out of several other VHDL data types.

IEEE 1164 Signals Values

IEEE 1164 standard defines nine-value signals:

U	Uninitialised
X	Forcing Unknown
0	Forcing 0
1	Forcing 1
Z	High Impedance
W	Weak Unknown
L	Weak 0
H	Weak 1
-	Don't Care

Library IEEE

The following modifications are required to make the previous entity declaration IEEE compliant.

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity half_adder is  
  Port ( x : in std_logic;  
        y : in std_logic;  
        sum : out std_logic;  
        carry : out std_logic);  
end half_adder;
```

Signal Mode

- ▶ Port declaration distinguishes between:
 - ▶ **in** - input signal
 - ▶ **out** - output signal
 - ▶ **inout** - bidirectional signal

Signal mode

```
entity half_adder is  
  Port ( x : in std_logic;
```

4 to 1 Multiplexer

This example uses `std_logic_vector(7 downto 0)`;

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity mux is  
  Port ( I0 : in std_logic_vector(7 downto 0);  
        I1 : in std_logic_vector(7 downto 0);  
        I2 : in std_logic_vector(7 downto 0);  
        I3 : in std_logic_vector(7 downto 0);  
        Sel : in std_logic_vector(1 downto 0);  
        Z : out std_logic_vector(7 downto 0));  
end mux;
```

Bit vector

std_logic_vector(7 downto 0)

entity mux is

```
Port ( I0 : in std_logic_vector(7 downto 0);
```

► This example refers to 8 bits long input vector.

► bit 7 - most significant bit

► bit 0 - least significant bit

Entity's Internal Behavior

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity half_adder is  
  Port ( x : in std_logic;  
        y : in std_logic;  
        sum : out std_logic;  
        carry : out std_logic);  
end half_adder;
```

```
architecture Behavioral of half_adder is  
  -- declaration  
begin  
  -- description of behavior  
end Behavioral;
```

VHDL describes
the internal
behavior in the
architecture
construct.

Architecture

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity half_adder is  
    Port ( x ,y: in std_logic;  
          sum,carry : out std_logic);  
end half_adder;
```

```
architecture concurrent_behavior of half_adder is  
begin
```

```
    sum <= (x xor y) after 5 ns;  
    carry <= (x and y) after 5 ns;  
end concurrent_behavior;
```