

# Arithmetic Circuit


► The arithmetic circuit may implemented with the following components:

► Parallel Adder

► Build from a cascade of full-adder circuits

► The data input to the parallel adder is manipulated in order to achieve a number of arithmetic operations

# N-bit Arithmetic/Logic Unit(ALU)

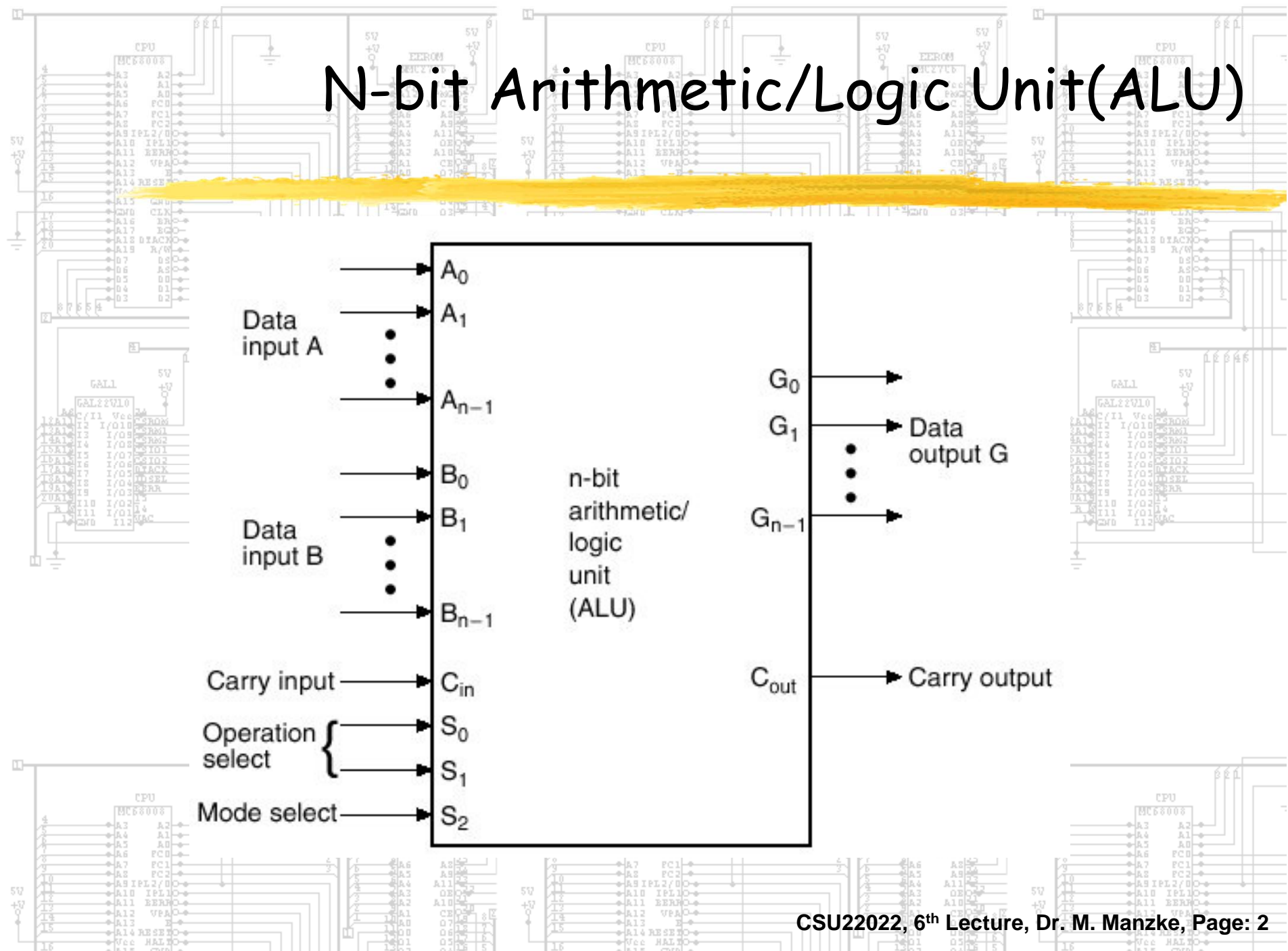

$$G = A + Y + C_{in}$$

► The arithmetic micro-ops can be implemented using the carry-in  $C_{in}$  and two select inputs  $S_1$  &  $S_0$ , which condition the  $B$  input to deliver  $Y$  to the full-adder computing:  $G = A + Y + C_{in}$ .

Select

Input

$S_1$

$S_0$

$Y$

$C_{in}=0$

$C_{in}=1$

0

0

all 0's

$G=A$

$G=A+1$

0

1

$\underline{B}$

$G=A+\underline{B}$

$G=A+\underline{B}+1$

1

0

$\underline{B}$

$G=A+\underline{B}$

$G=A+\underline{B}+1$

1


1

all 1's

$G=A-1$

$G=A$

# Arithmetic Circuit

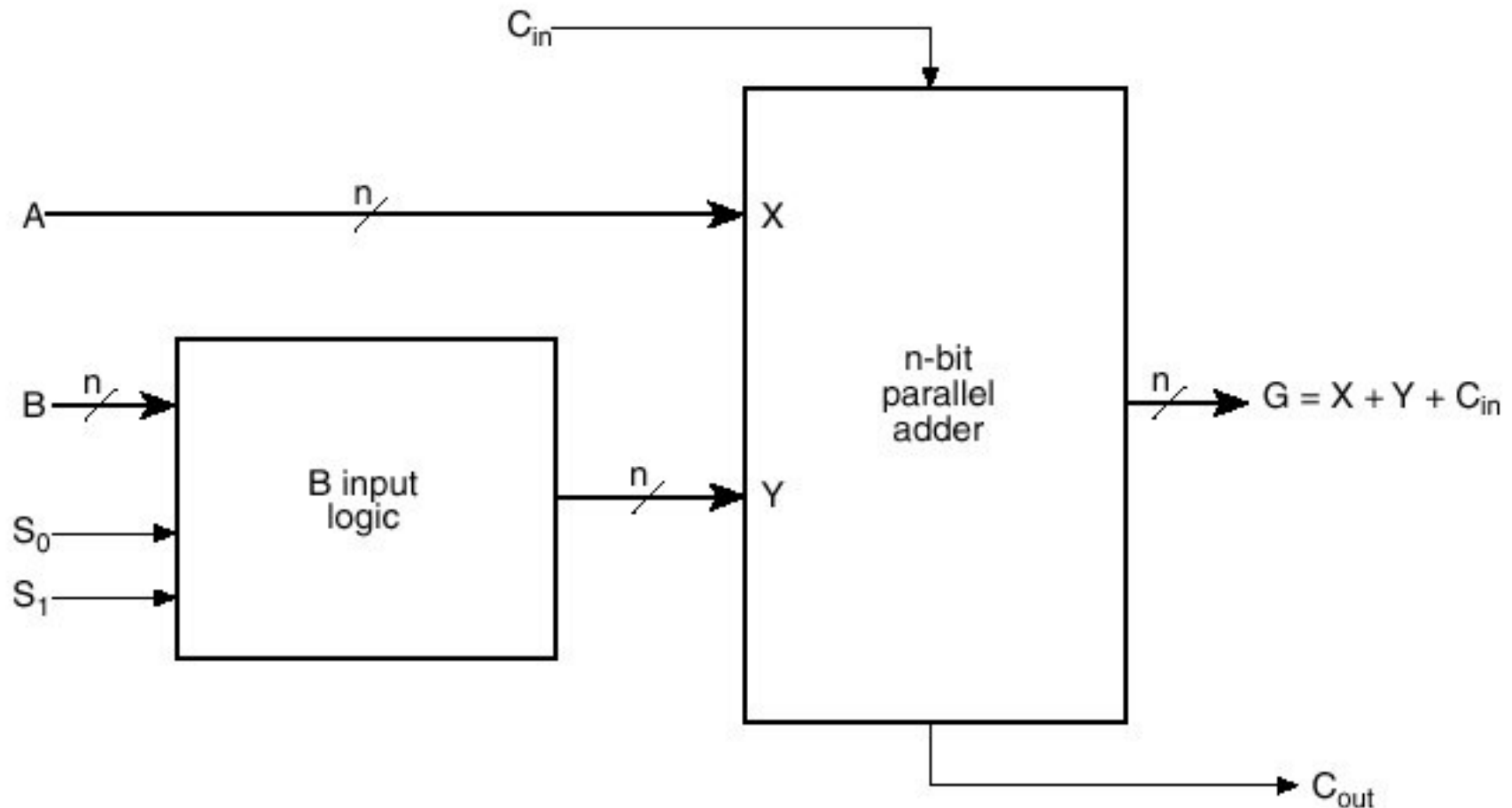

$Y(S,B)$

► The logic function  $Y(S,B)$  is derived as:

		$S_0$			
		00	01	11	10
$S_1$	0			1	
	1	1		1	1
		$B_i$			


$$Y_i = S_0 B_i + S_1 \bar{B}_i$$

► Thus a 2:1 MUX controlled by  $B_i$  can efficiently generates  $Y_i$



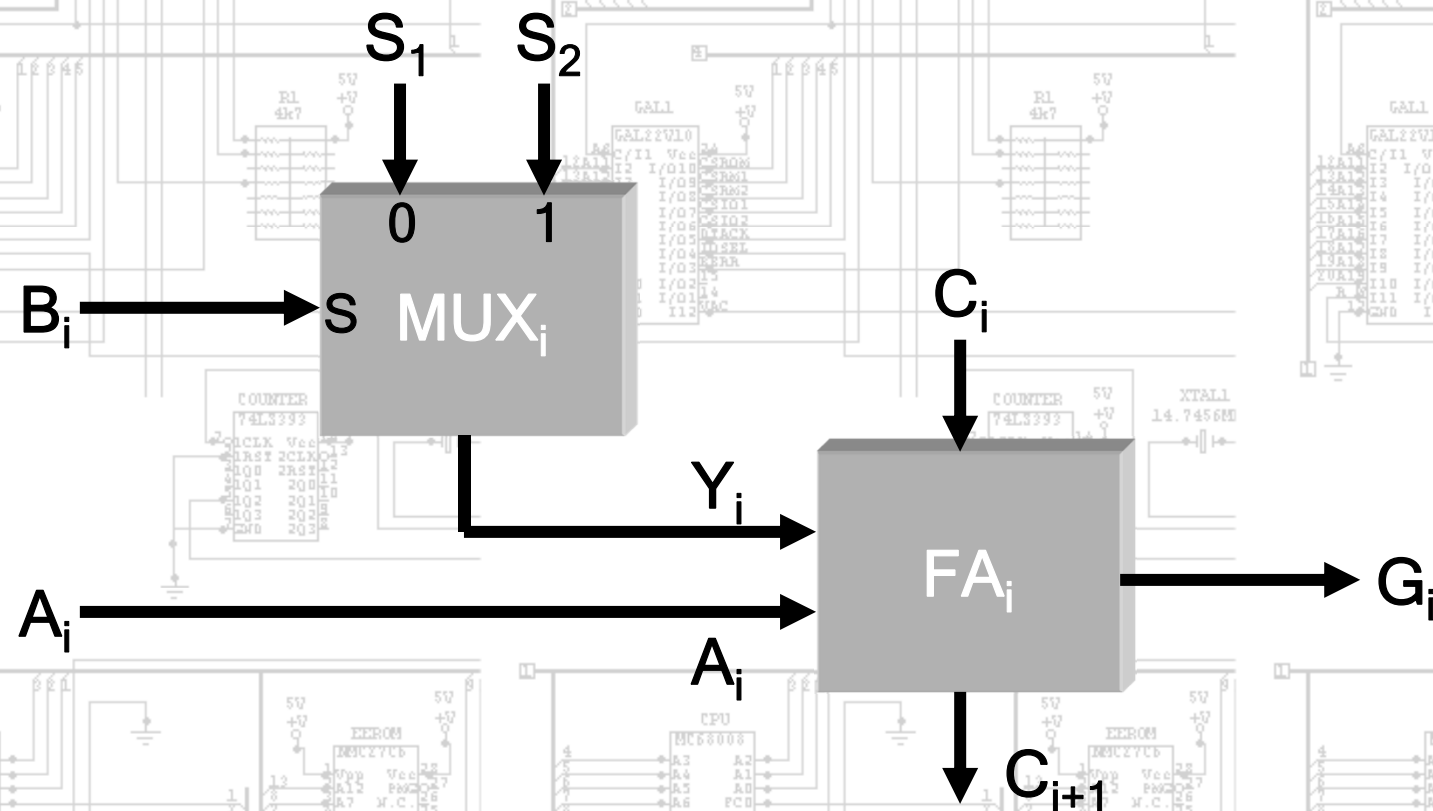
# One Bit Slice

▶ One bit slice of the Arithmetic unit on the next slide.



# 4-Bit Arithmetic Circuit

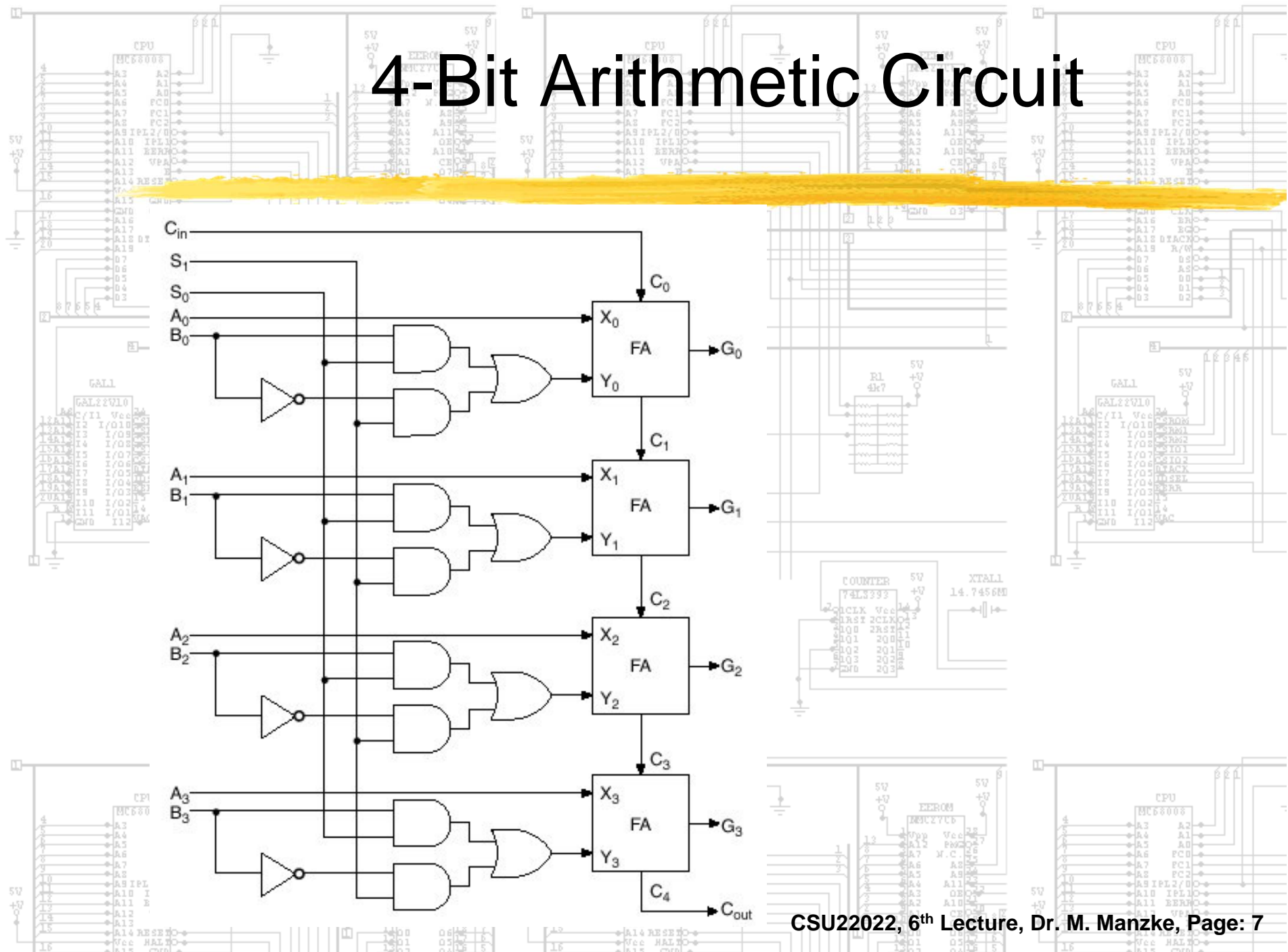

# Logic Circuit

▶ The logic function are similarly selected by input  $S_1$  and  $S_0$ :

Select

Output

$S_1$

$S_0$

0

0

$G = A \wedge B$

AND

0

1

$G = A \vee B$

OR

1

0

$G = \underline{A} \oplus B$

XOR

1


1

$G = \underline{A}$

NOT


 
# Logic Circuit Implemented with a 4:1 MUX




One bit slice of the logic unit.

# ALU (Arithmetic/Logic)


► We next use an additional 2:1 MUX controlled by  $S_2$  to select either the arithmetic output bit or the logic output bit as shown on the next slide.

# One bit slice ALU

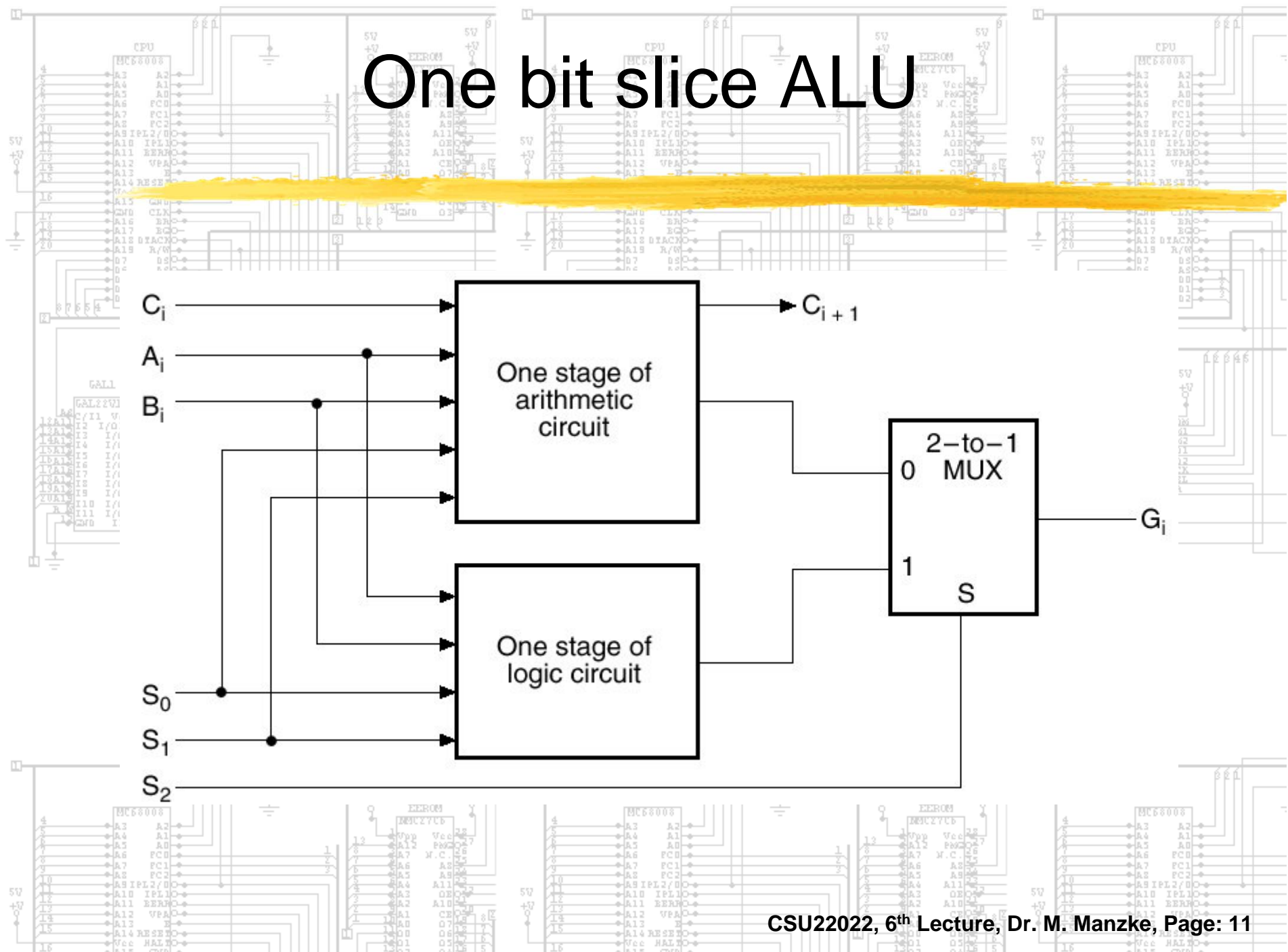
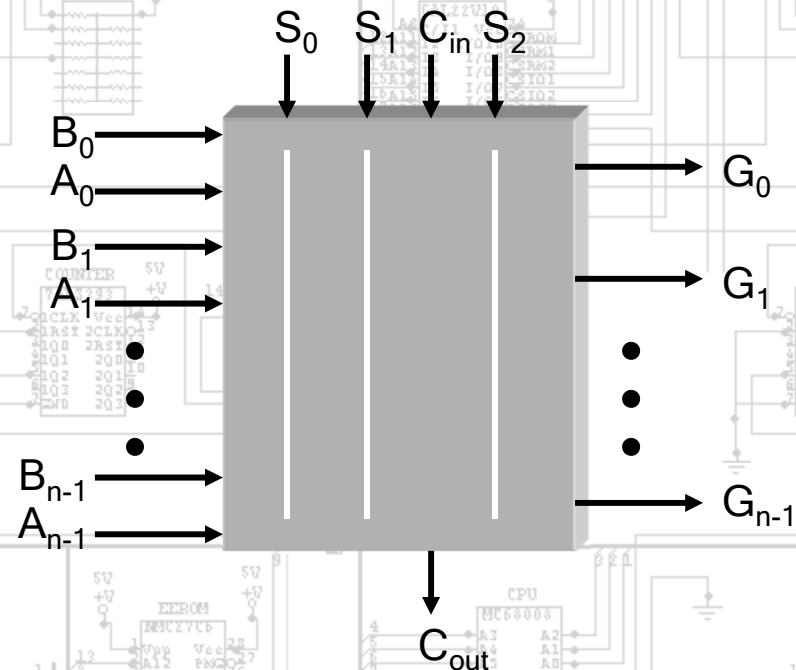
# N-bit ALU

To construct an n-bit ALU we concatenate n-bit slices together:



# Physical Implementation

Physical schematic of an n-bit ALU assembled from a bit slices as shown on the previous slide.

1. Note the control signals, because they apply to the whole word, tend to cross the datapath.

2. This geometry results in very efficient VLSI chip implementation.



# Adder

▶ This adder gives us a fast combinational ALU with the following functionality:

Select

$S_2$

$S_1$

$S_0$

Output

$C_{in}$

0

0

0

0

$G = A$

TRANSFER

0

0

0

1

$G = A + 1$

INCREMENT

0

0

1

0

$G = A + B$

ADD

0

0

1

1

$G = A + B + 1$

ADD WITH C

0

1

0

0

$G = A + \overline{B}$

A plus 1's C.B

0

1

0

1

$G = A + B + 1$

SUBTRACT

0

1

1

0

$G = A - 1$

DECREMENT

0

1

1

1

$G = A$

TRANSFER

1

0

0

X

$G = A \wedge B$

AND

1

0

1

X

$G = A \vee B$

OR

1

1

0

X

$G = A \oplus B$

XOR

1

1

1

X

$G = A$

NOT

# 4-Bit SR/SL Shifter Unit

For speed of execution the shifter unit is always implemented as a combinational circuit based on a MUX:

